


Fig. 2: Heater Circuit

## ANTI-LOCK BRAKES



# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

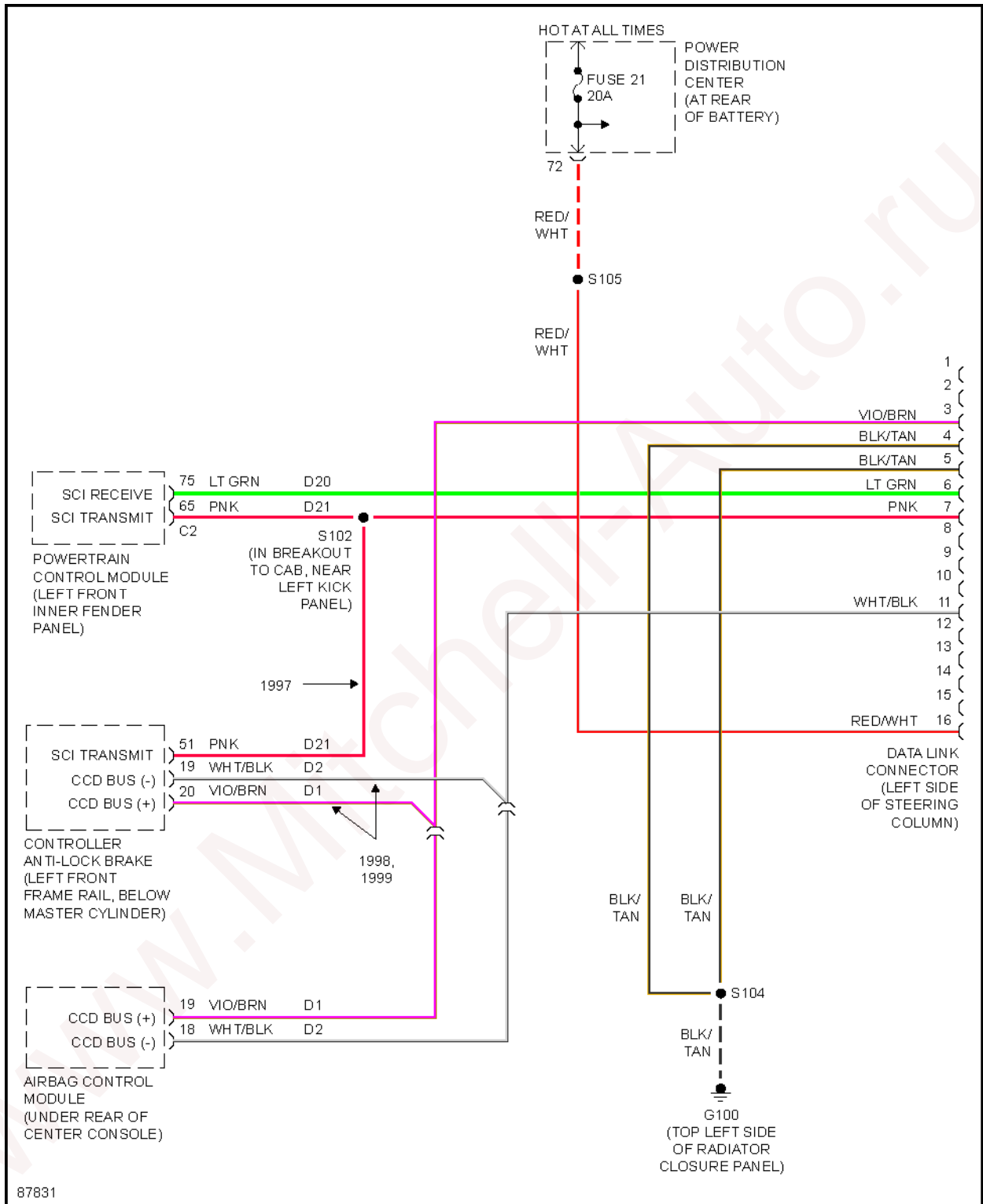


**Fig. 4: Computer Data Lines**

### COOLING FAN

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

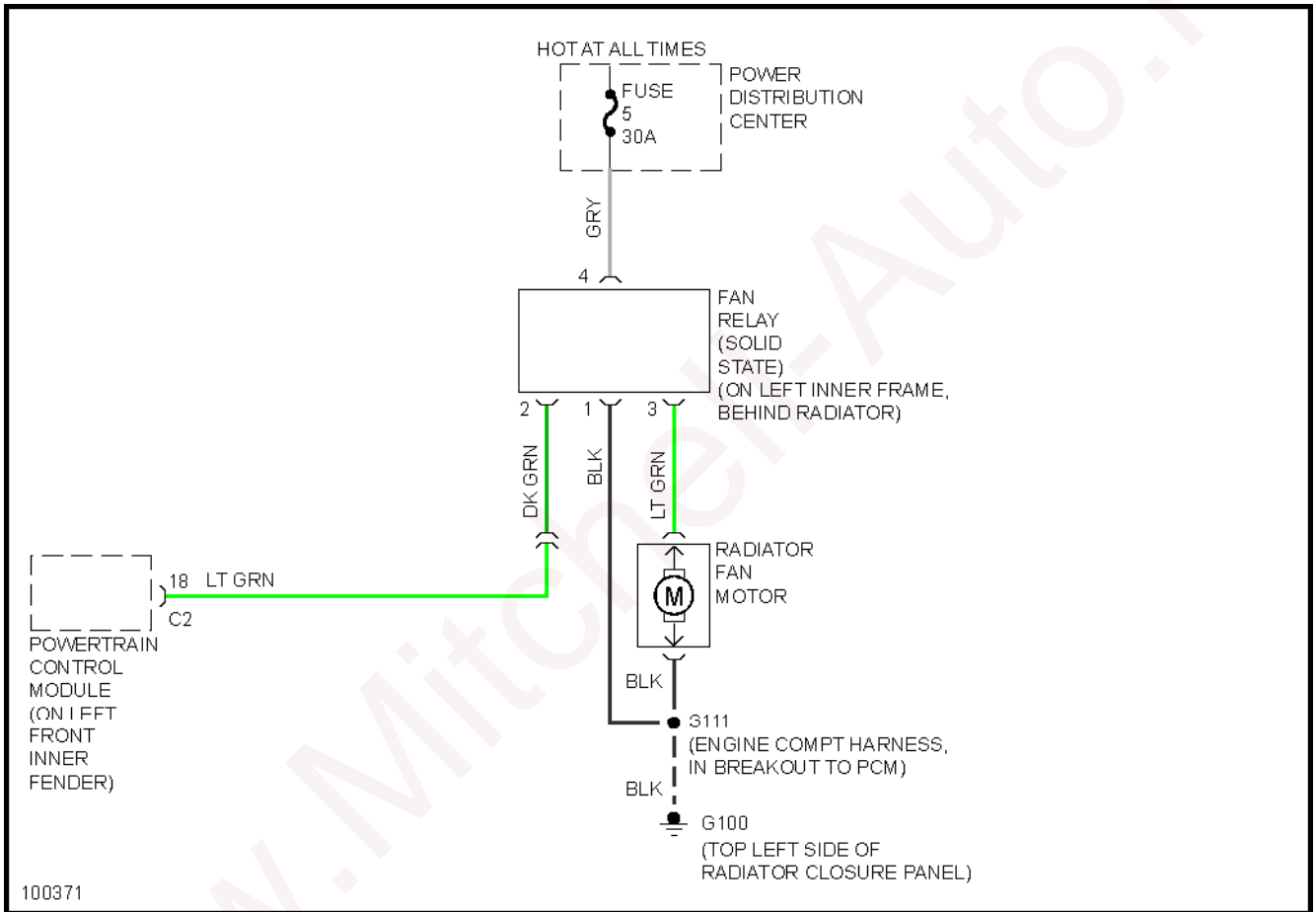


**Fig. 5: Cooling Fan Circuit**

## CRUISE CONTROL

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

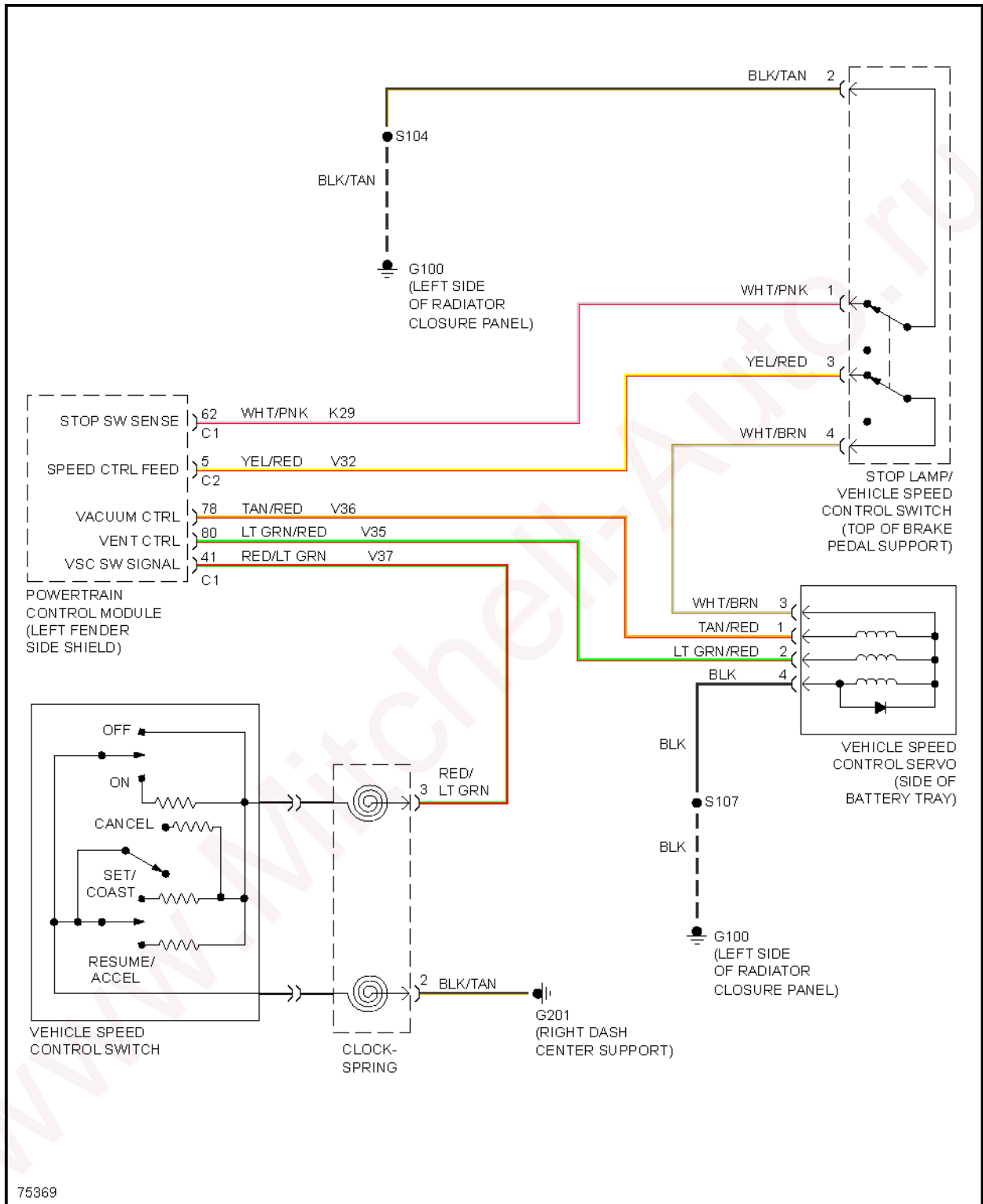


**Fig. 6: Cruise Control Circuit**

### DEFOGGERS

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

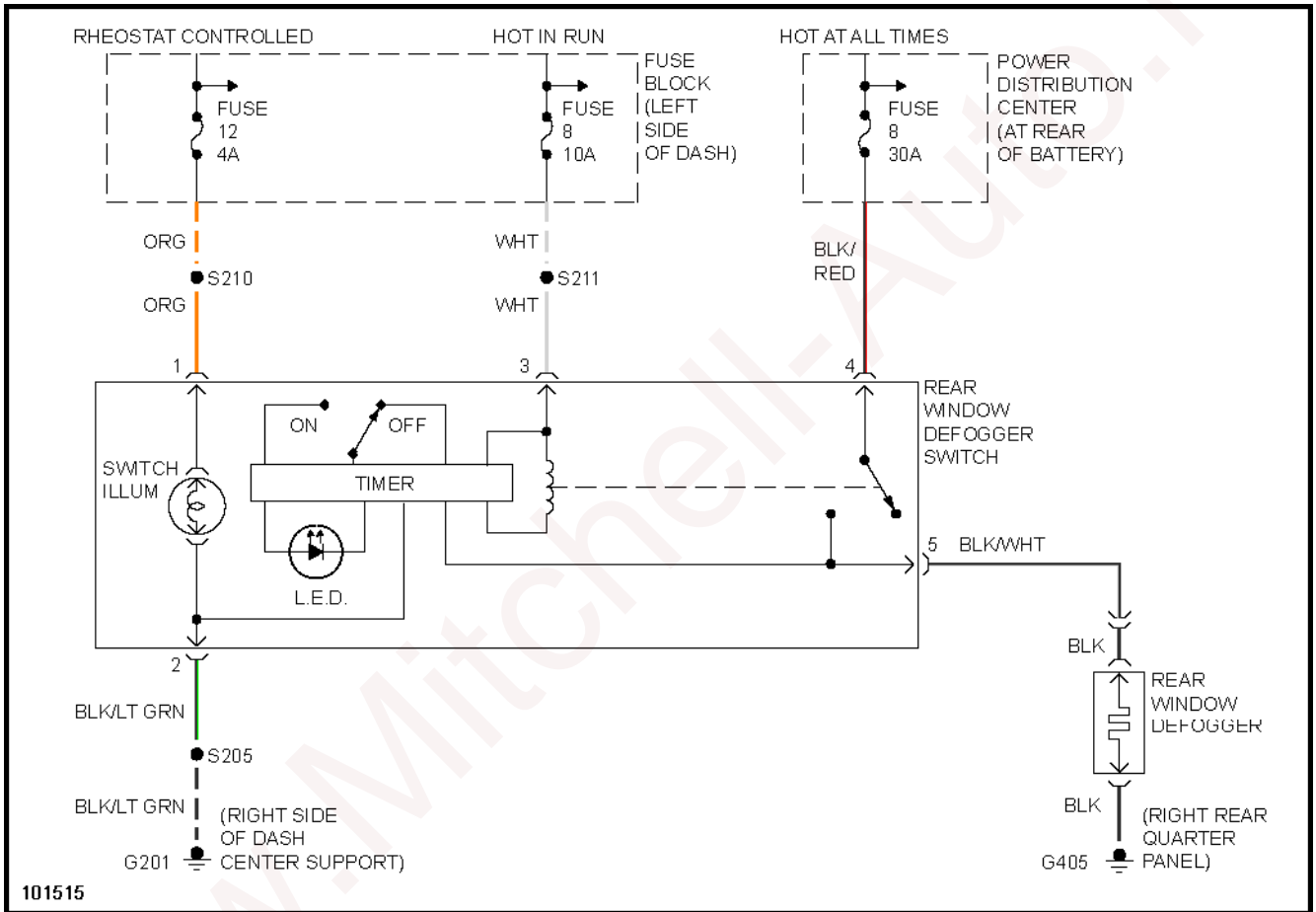

**Fig. 7: Defogger Circuit**

## ENGINE PERFORMANCE

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

### 2.0L

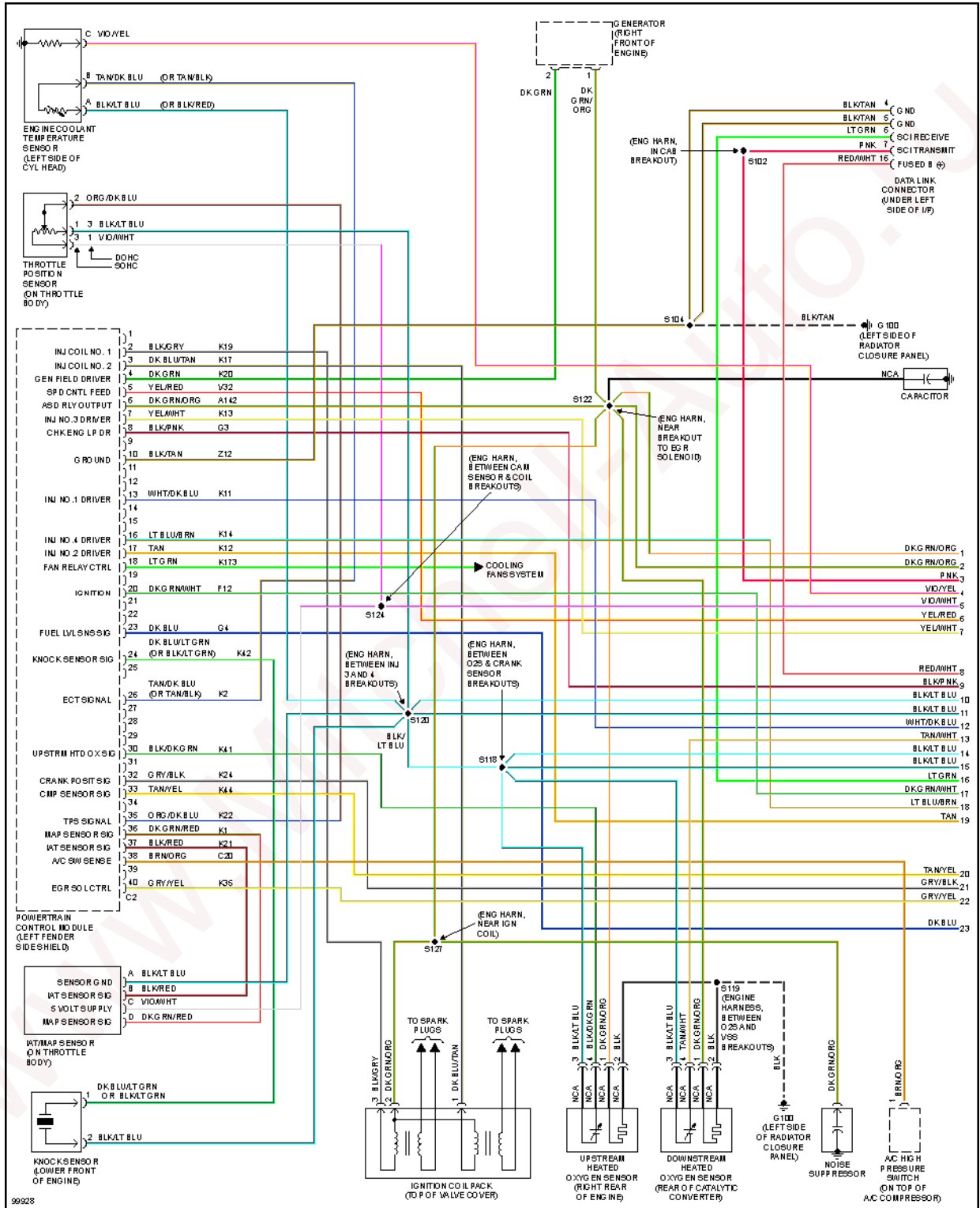


Fig. 8: 2.0L, Engine Performance Circuits (1 of 3)



# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

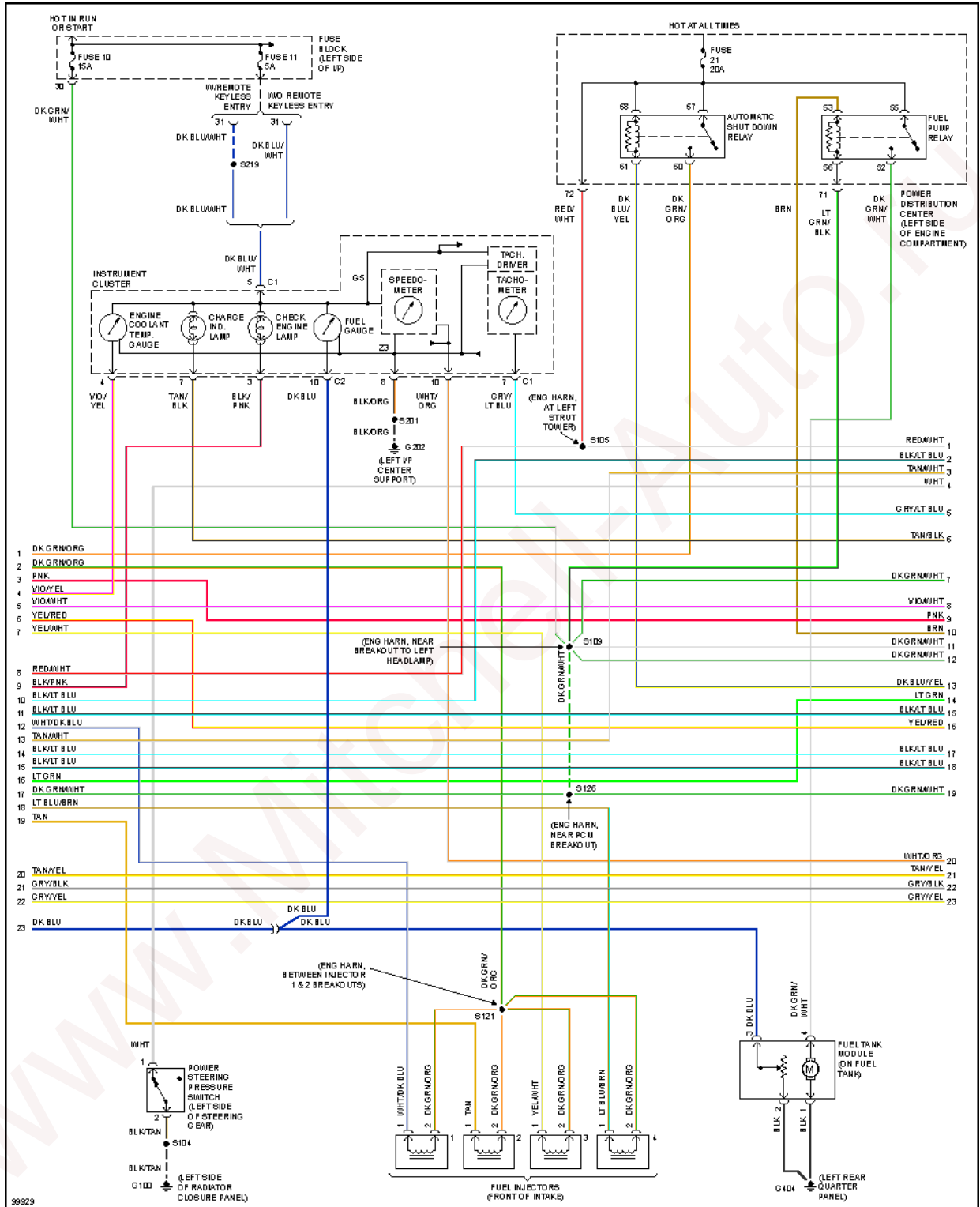


Fig. 9: 2.0L, Engine Performance Circuits (2 of 3)

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon


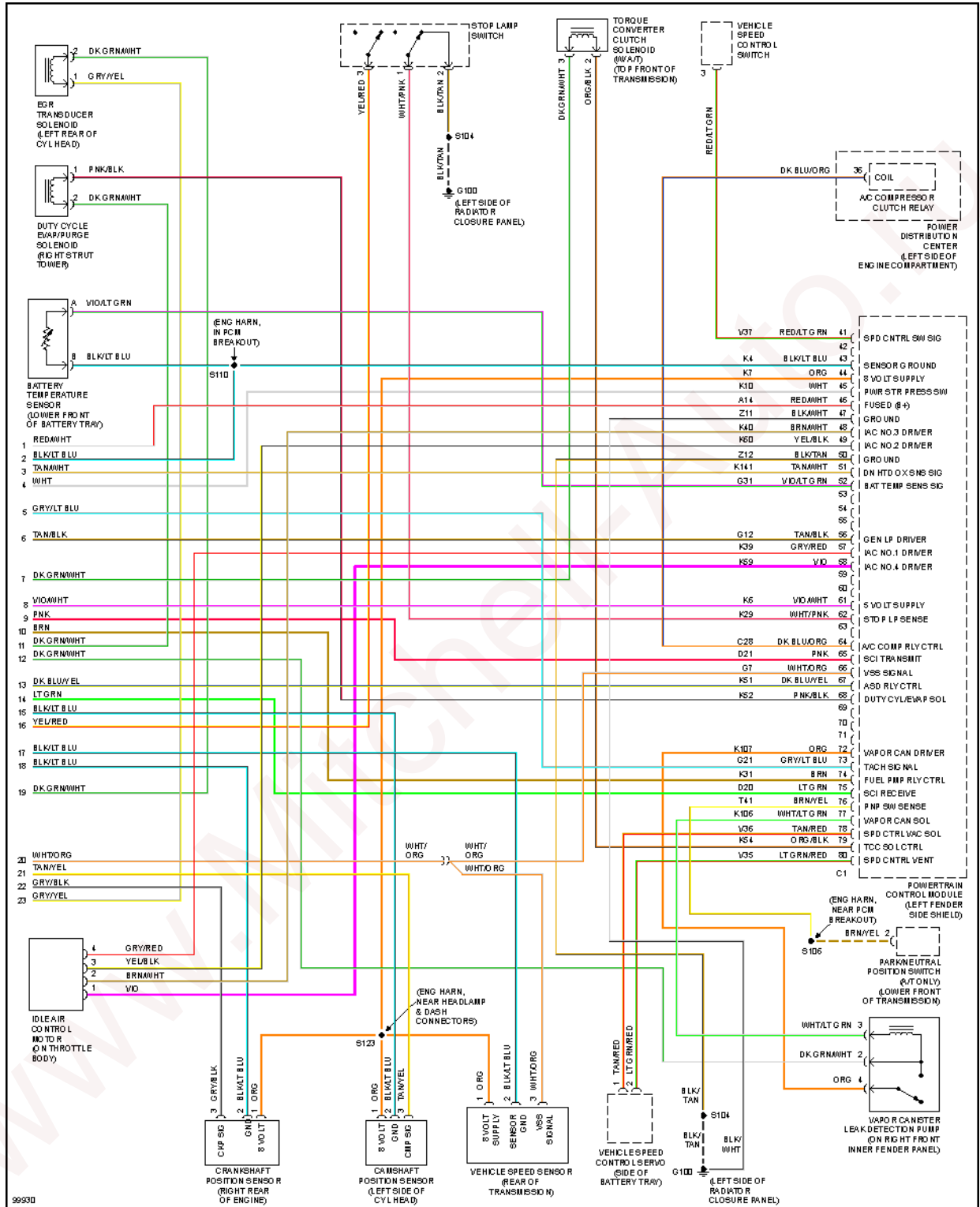


Fig. 10: 2.0L, Engine Performance Circuits (3 of 3)

## EXTERIOR LIGHTS

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

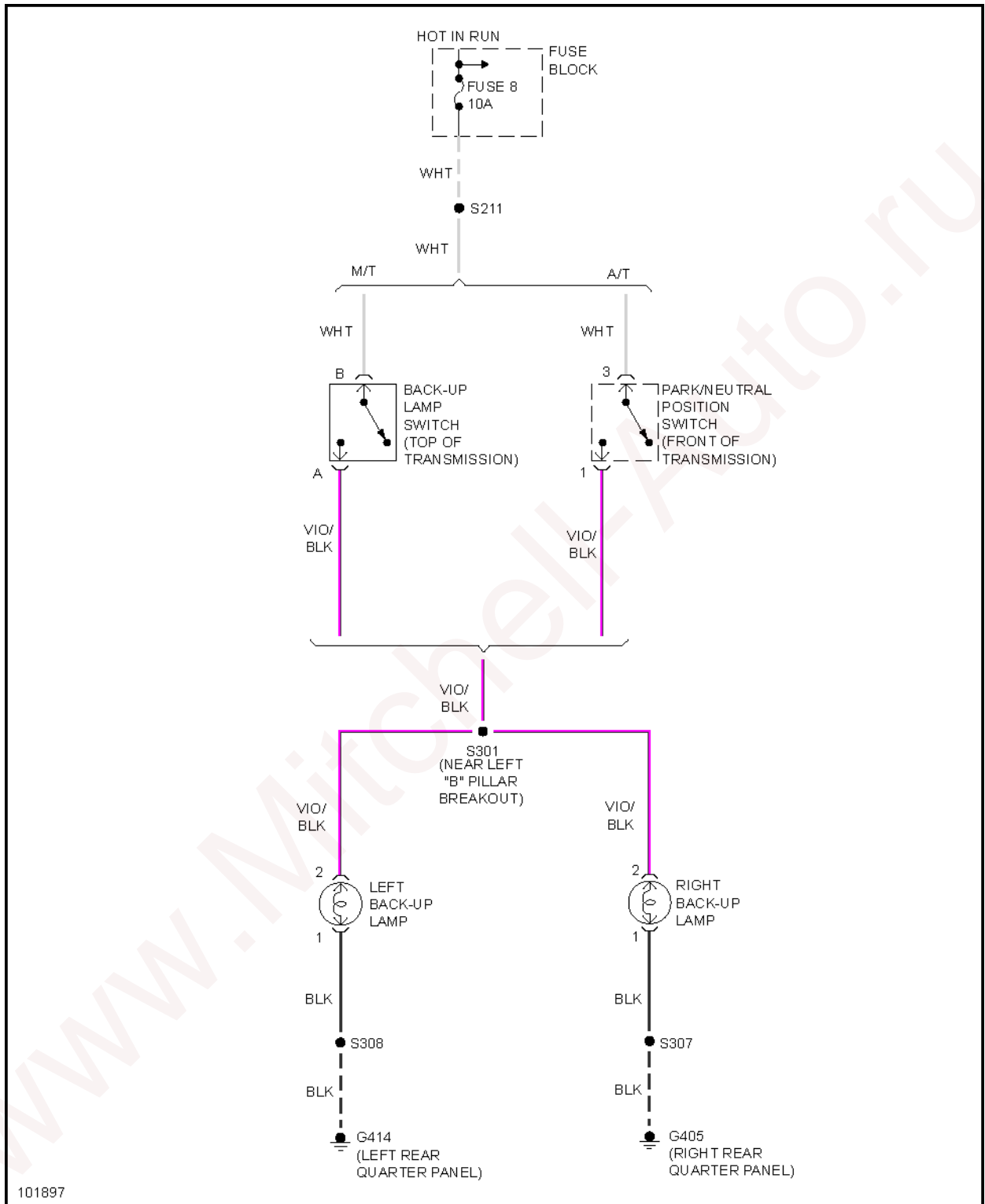

**Fig. 11: Back-up Lamps Circuit**

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

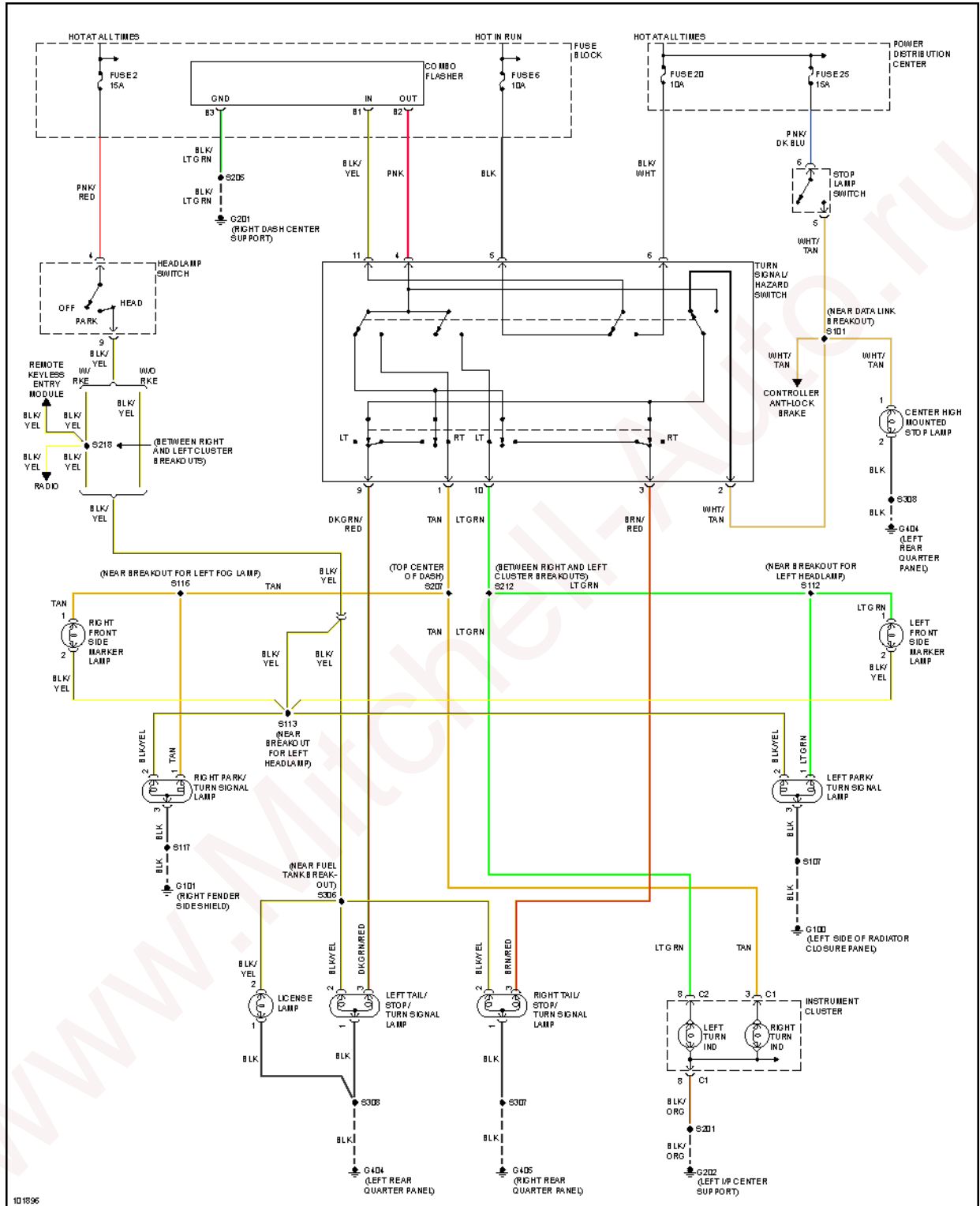


Fig. 12: Exterior Lamps Circuit

### GROUND DISTRIBUTION

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

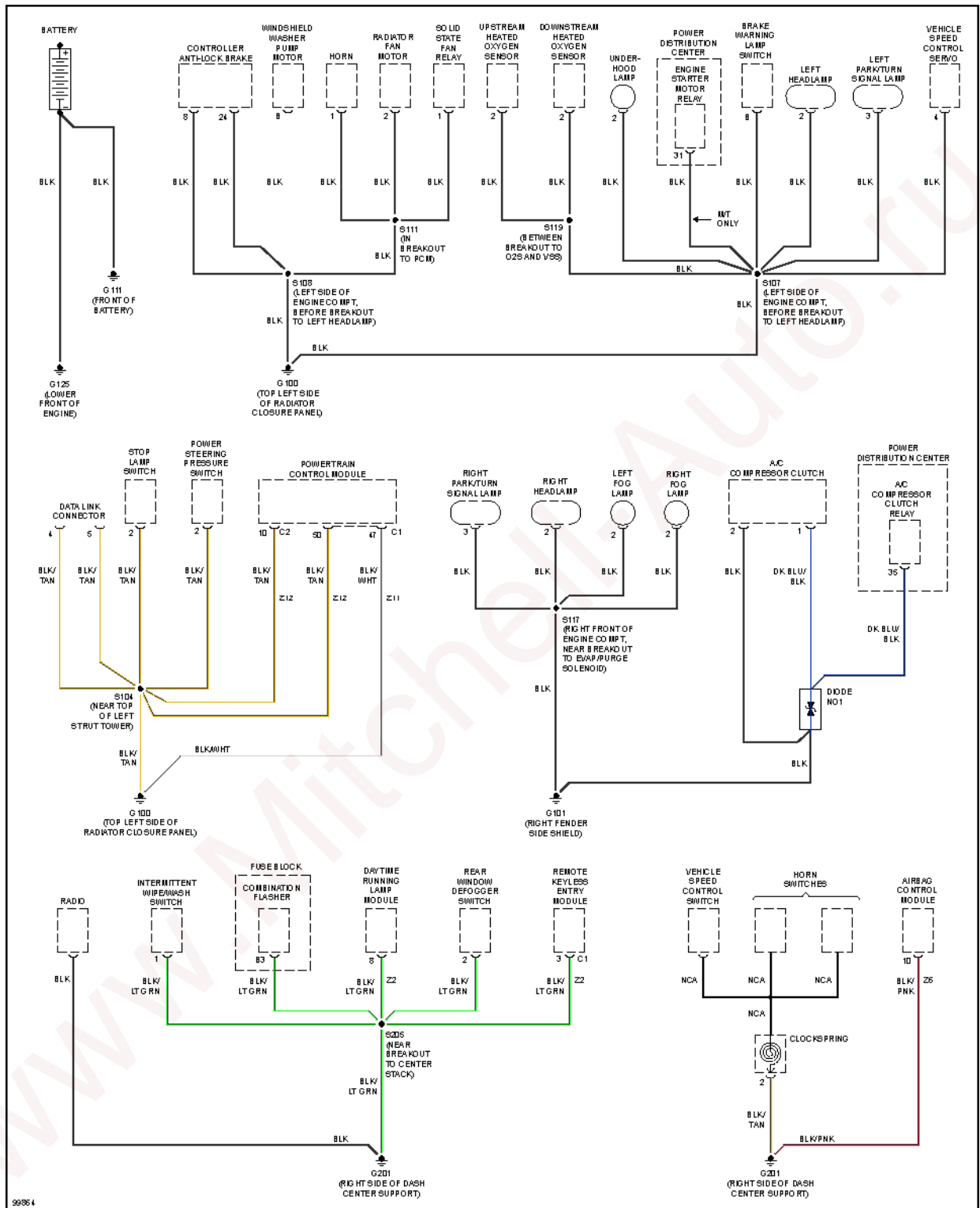


Fig. 13: Ground Distribution Circuit (1 of 2)

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

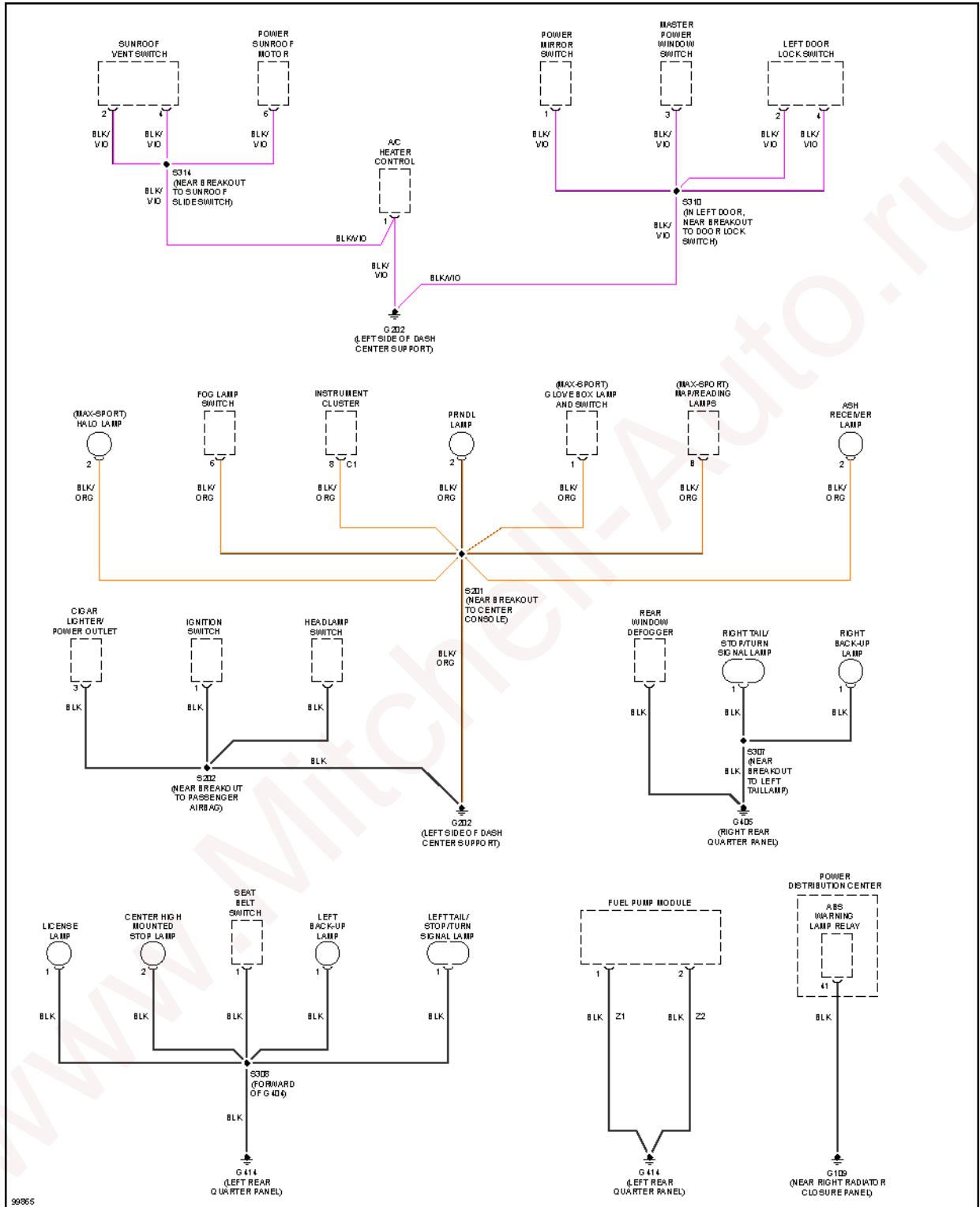


Fig. 14: Ground Distribution Circuit (2 of 2)

### HEADLIGHTS

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

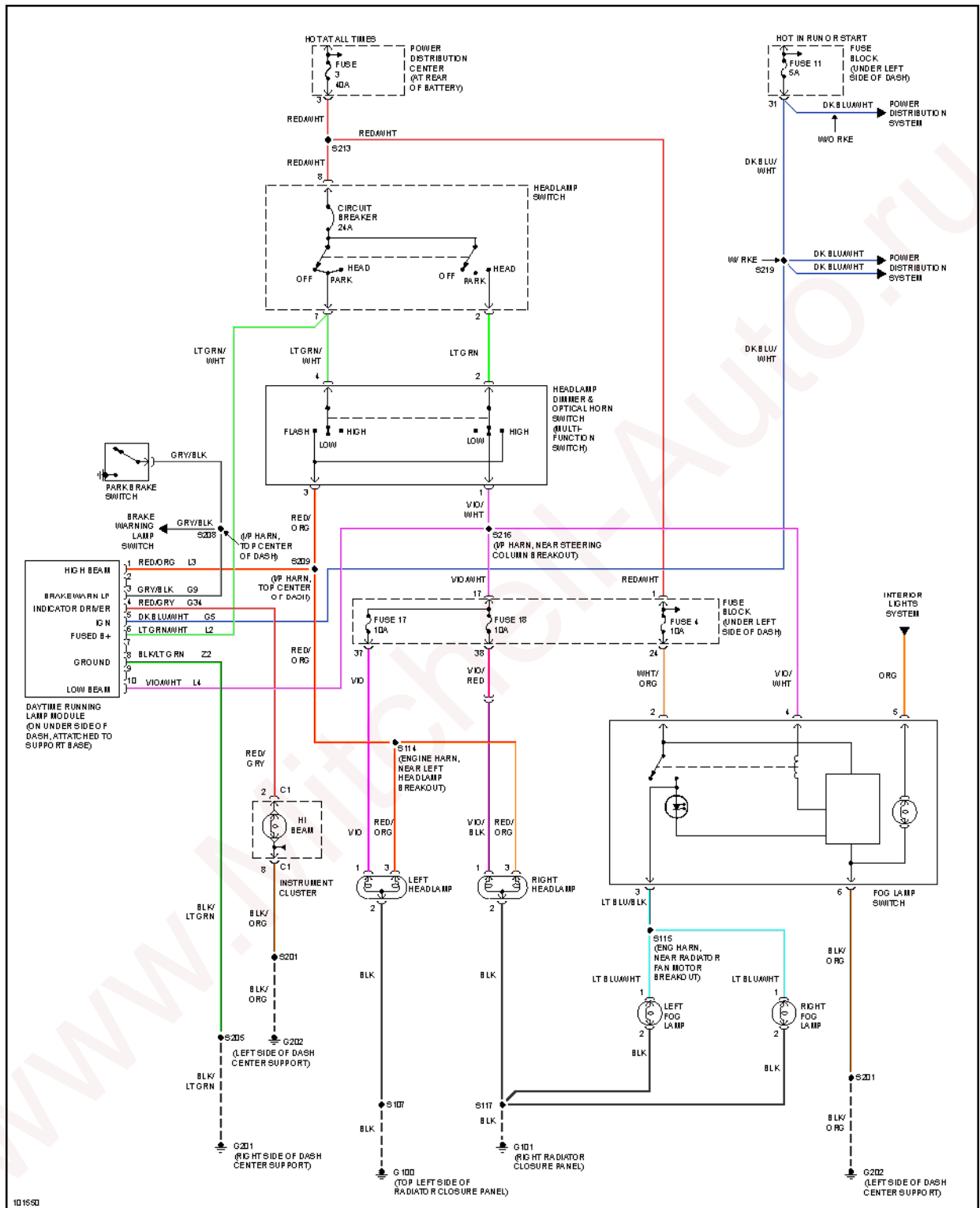


Fig. 15: Headlamps/Fog Lamps Circuit, W/ DRL

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

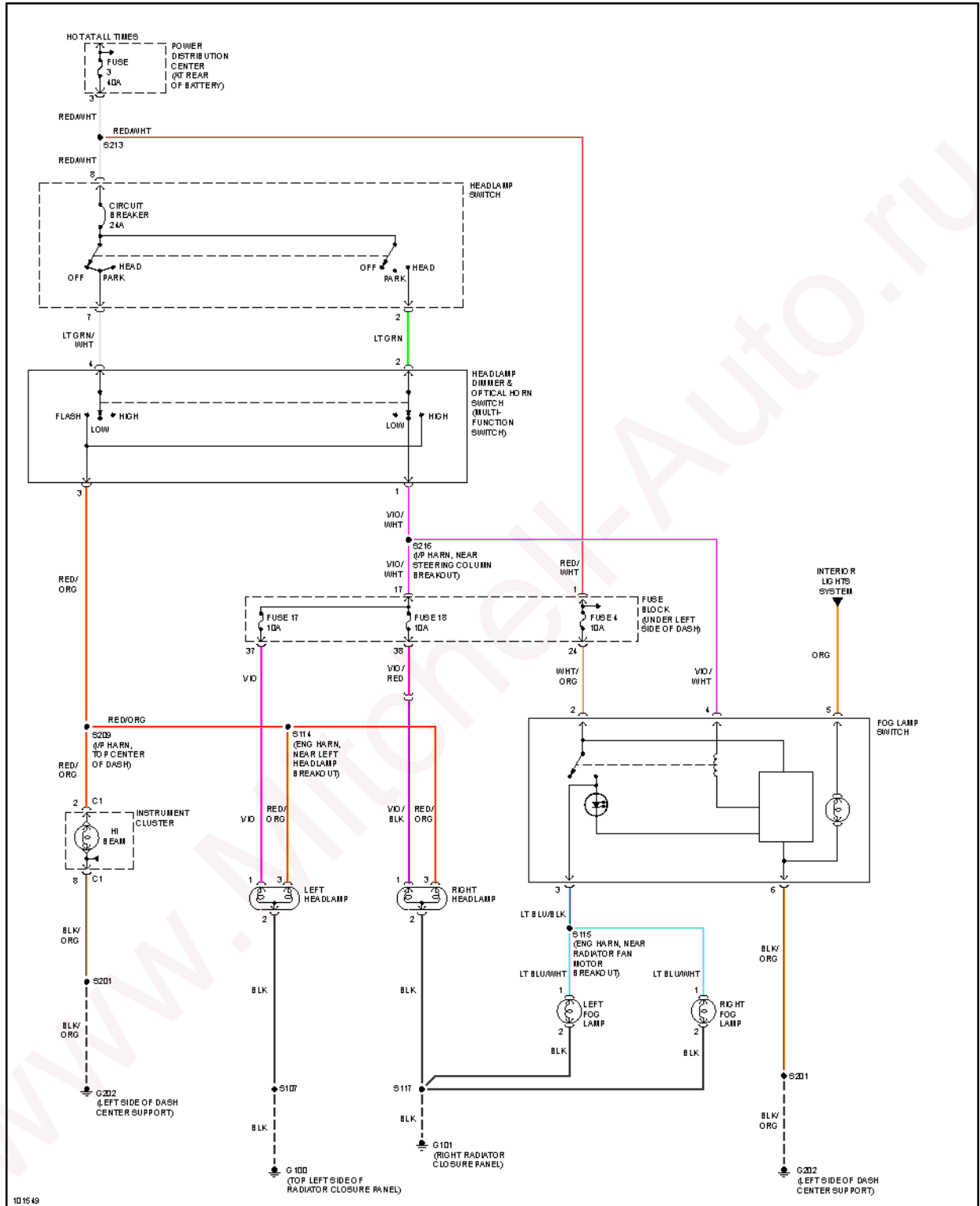


Fig. 16: Headlamps/Fog Lamps Circuit, W/O DRL

### HORN



# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

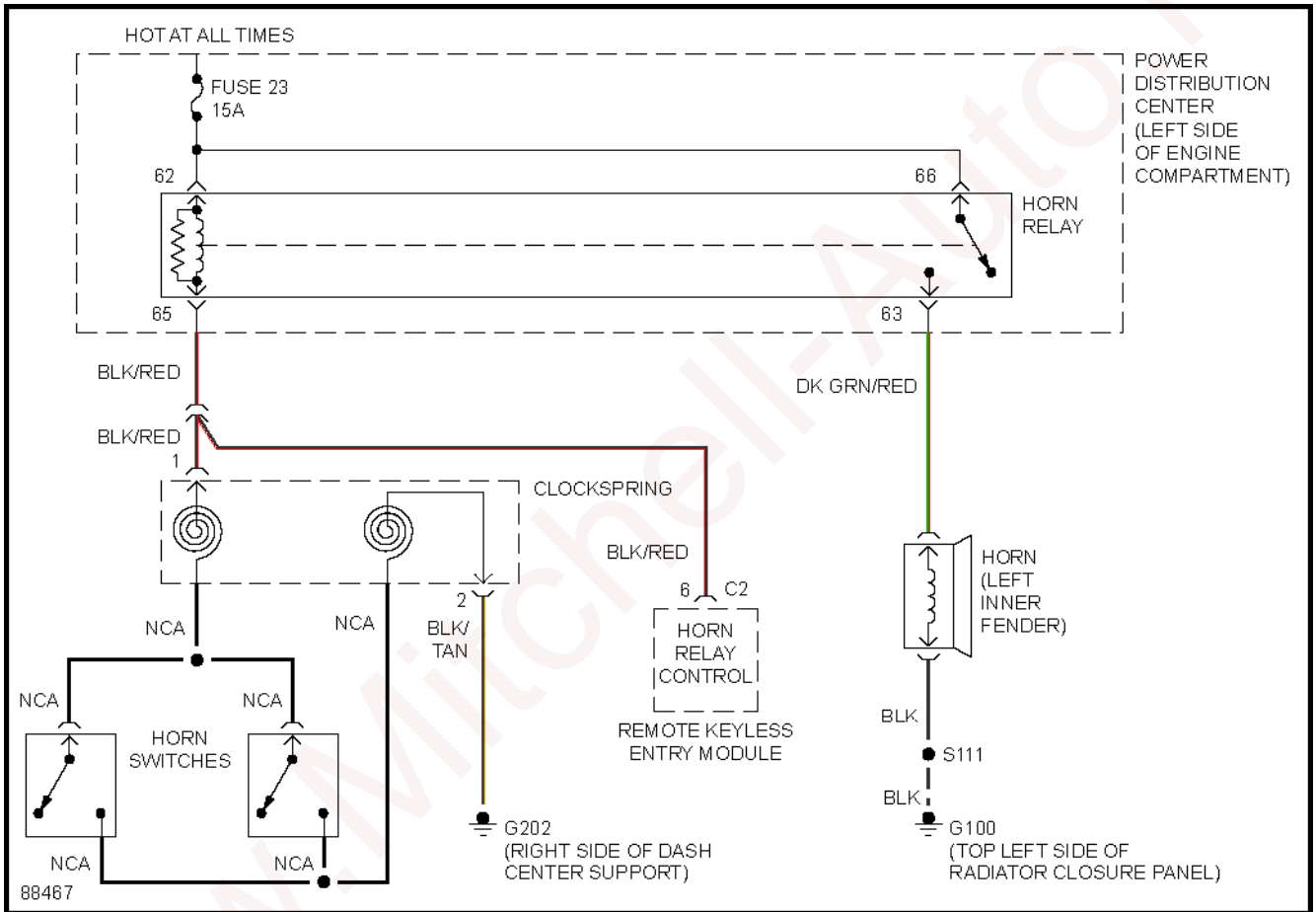


Fig. 17: Horn Circuit

## INSTRUMENT CLUSTER

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

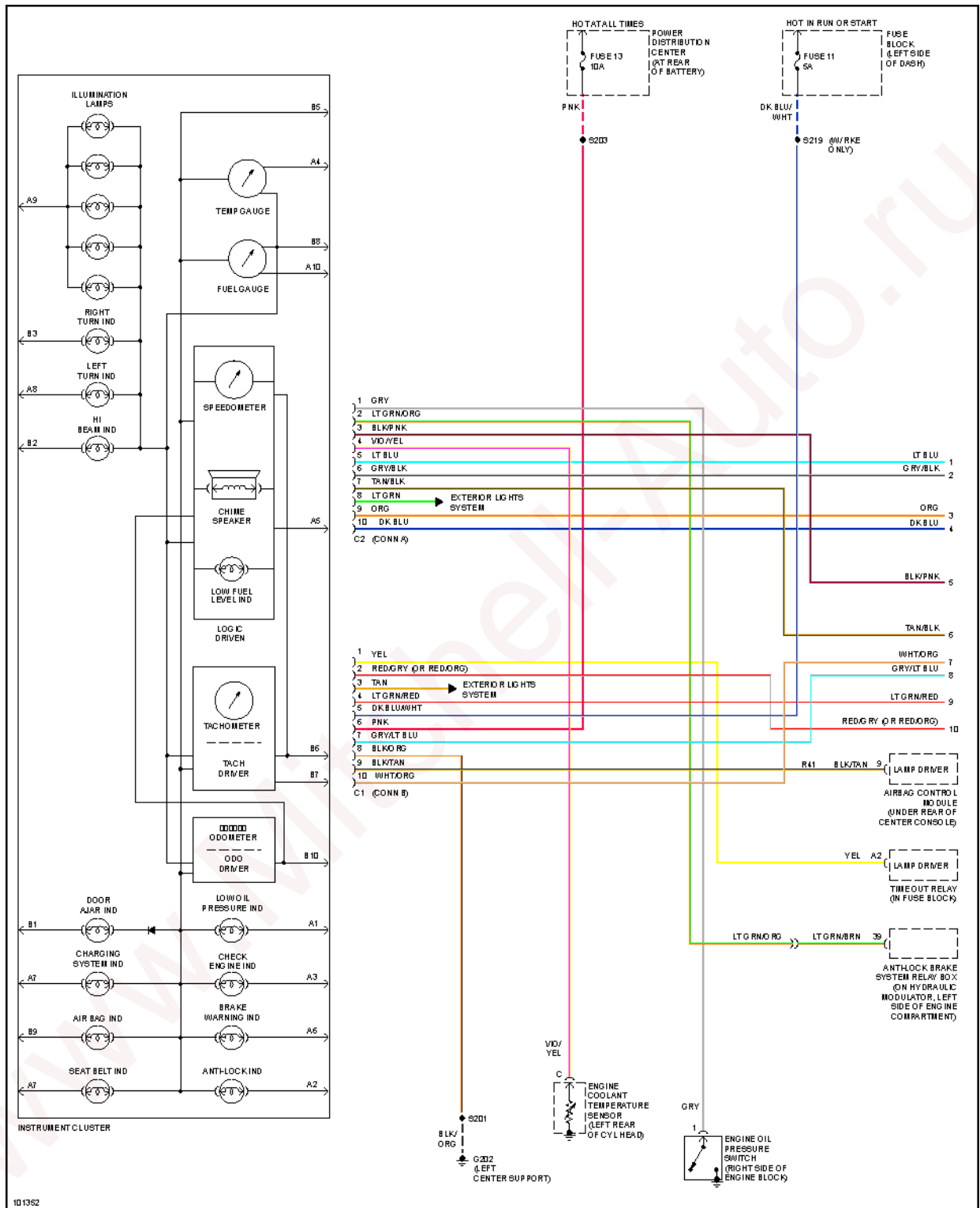


Fig. 18: Instrument Cluster Circuit (1 of 2)

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

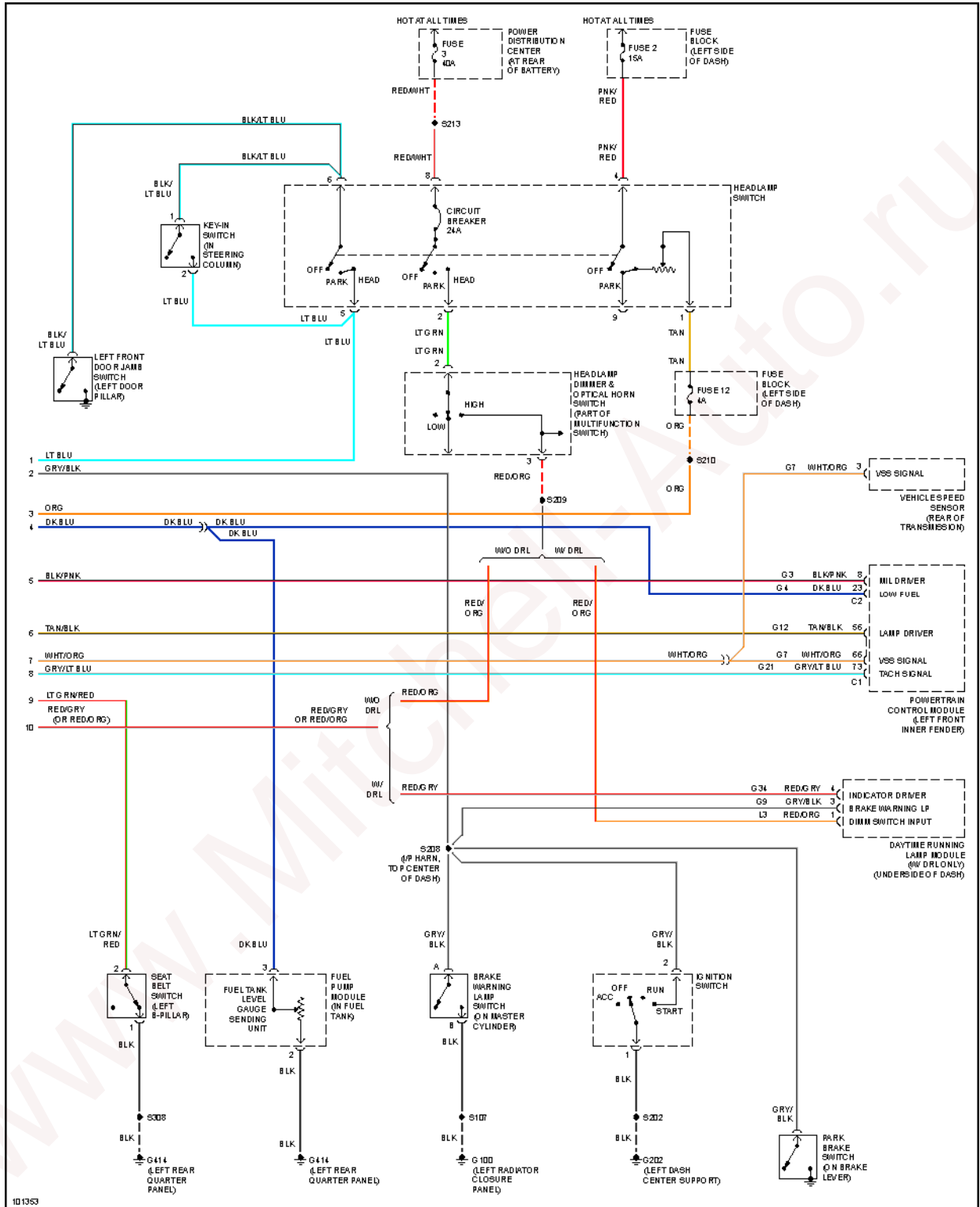


Fig. 19: Instrument Cluster Circuit (2 of 2)

## INTERIOR LIGHTS



# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

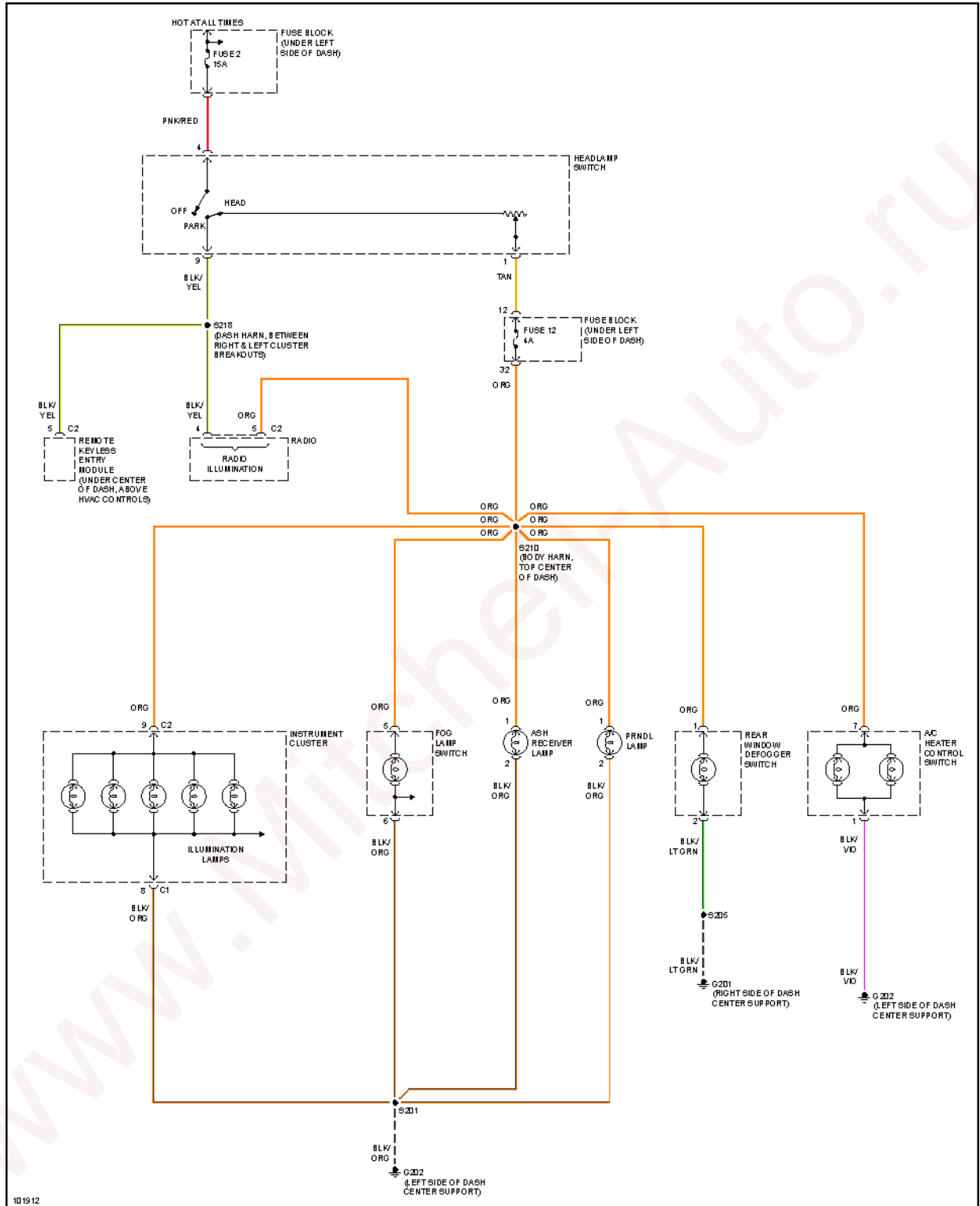


Fig. 21: Instrument Illumination Circuit

### POWER DISTRIBUTION

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

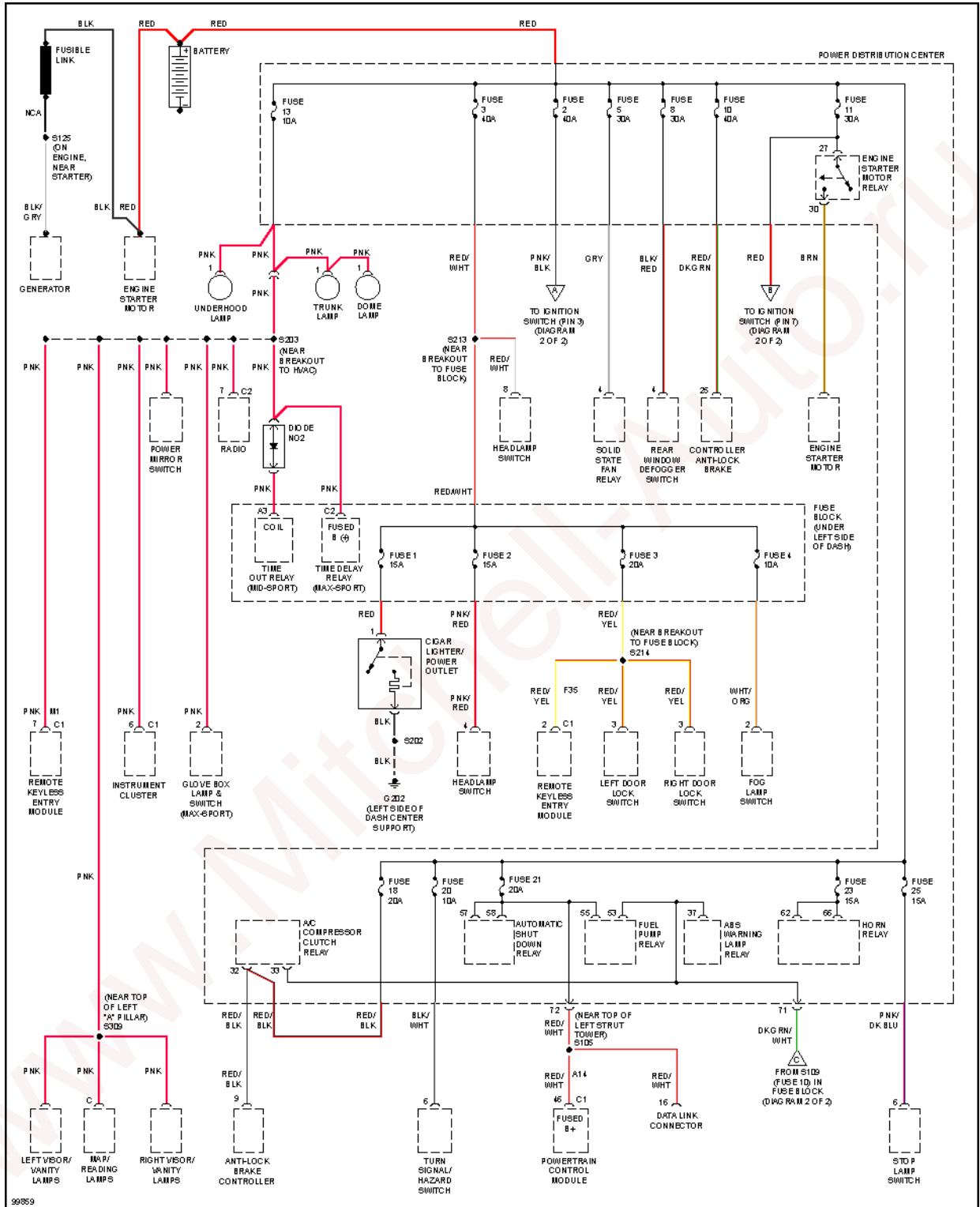


Fig. 22: Power Distribution Circuit (1 of 2)

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon


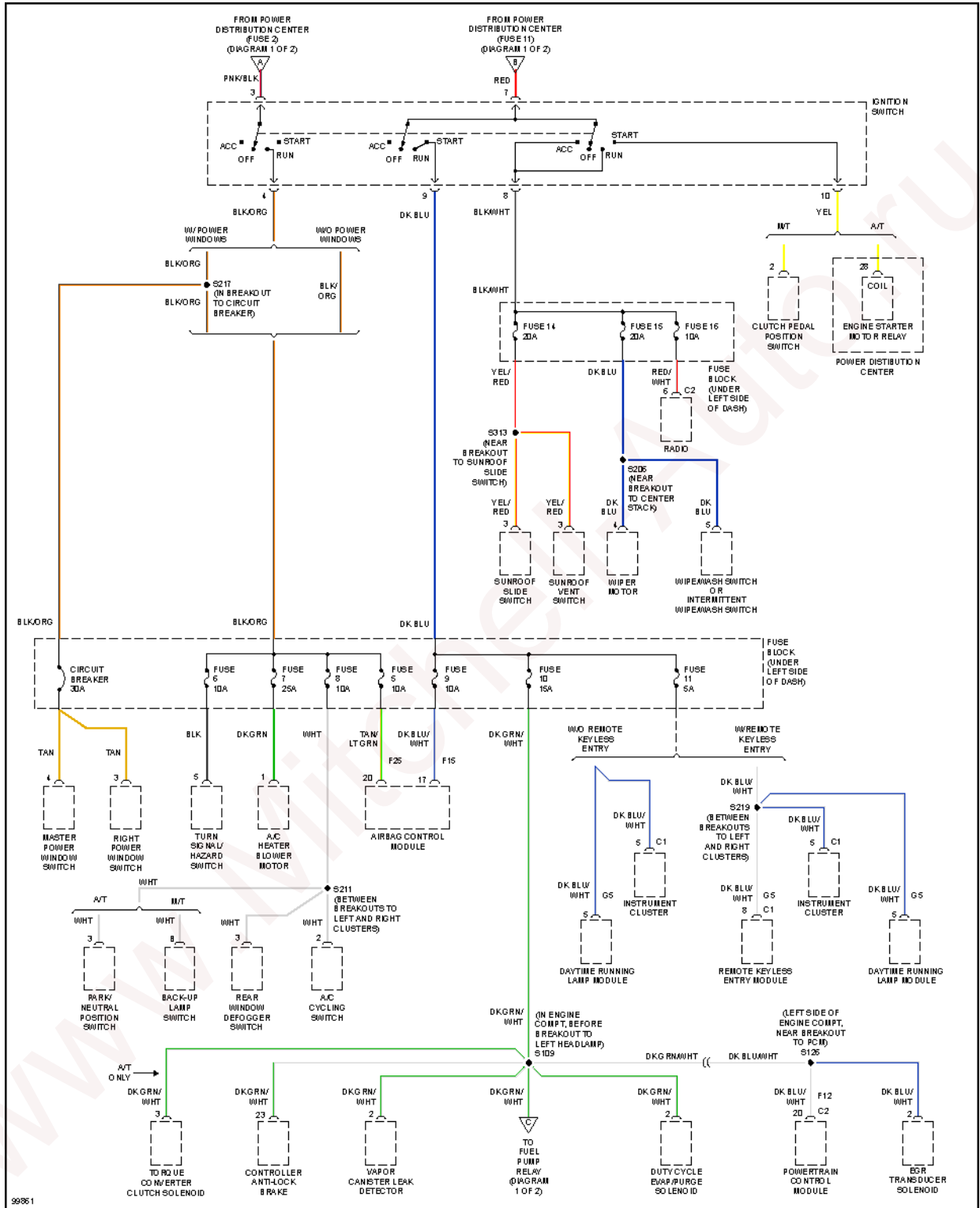


Fig. 23: Power Distribution Circuit (2 of 2)

### POWER DOOR LOCKS

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

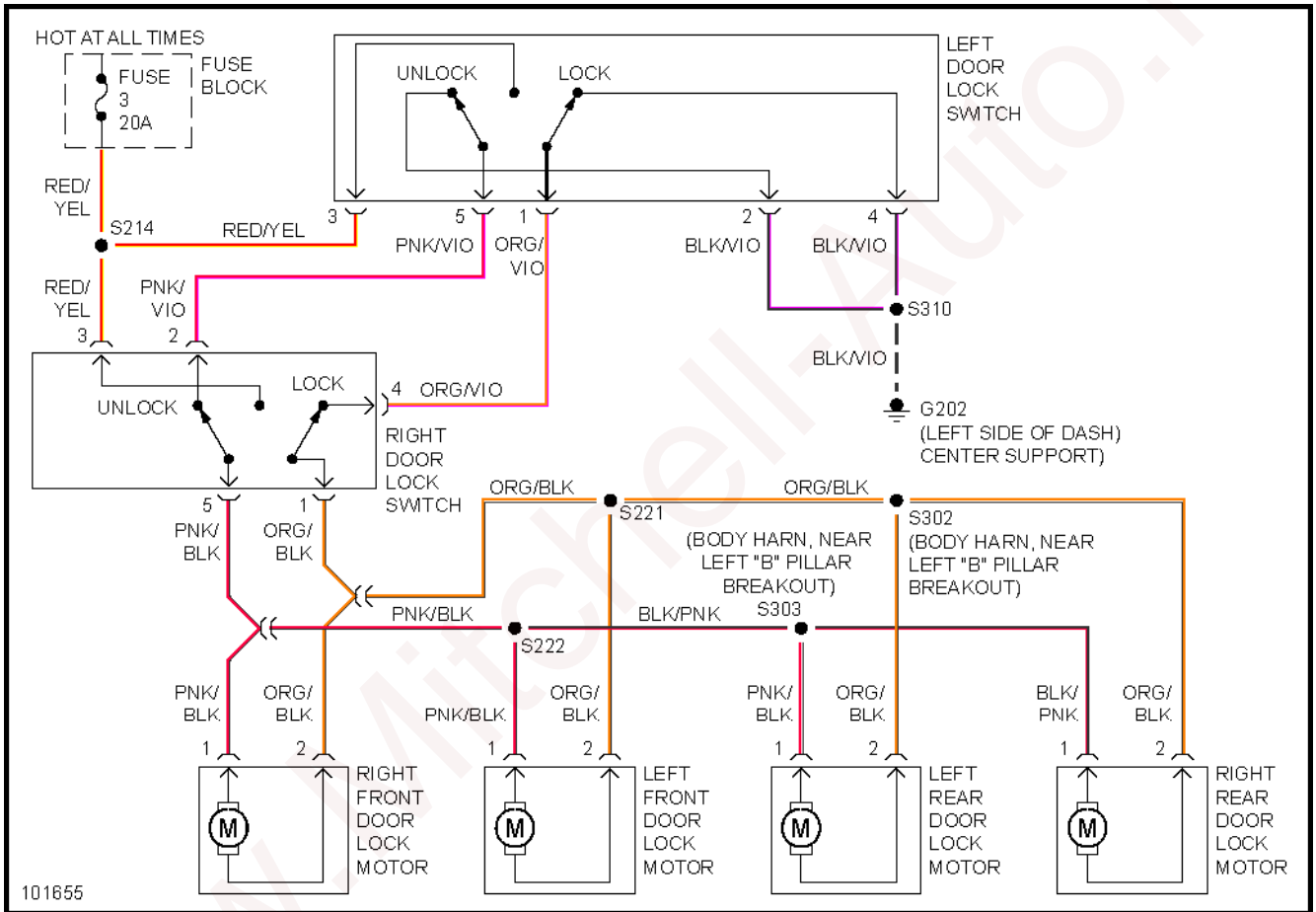

**Fig. 24: Door Lock Circuit**



# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

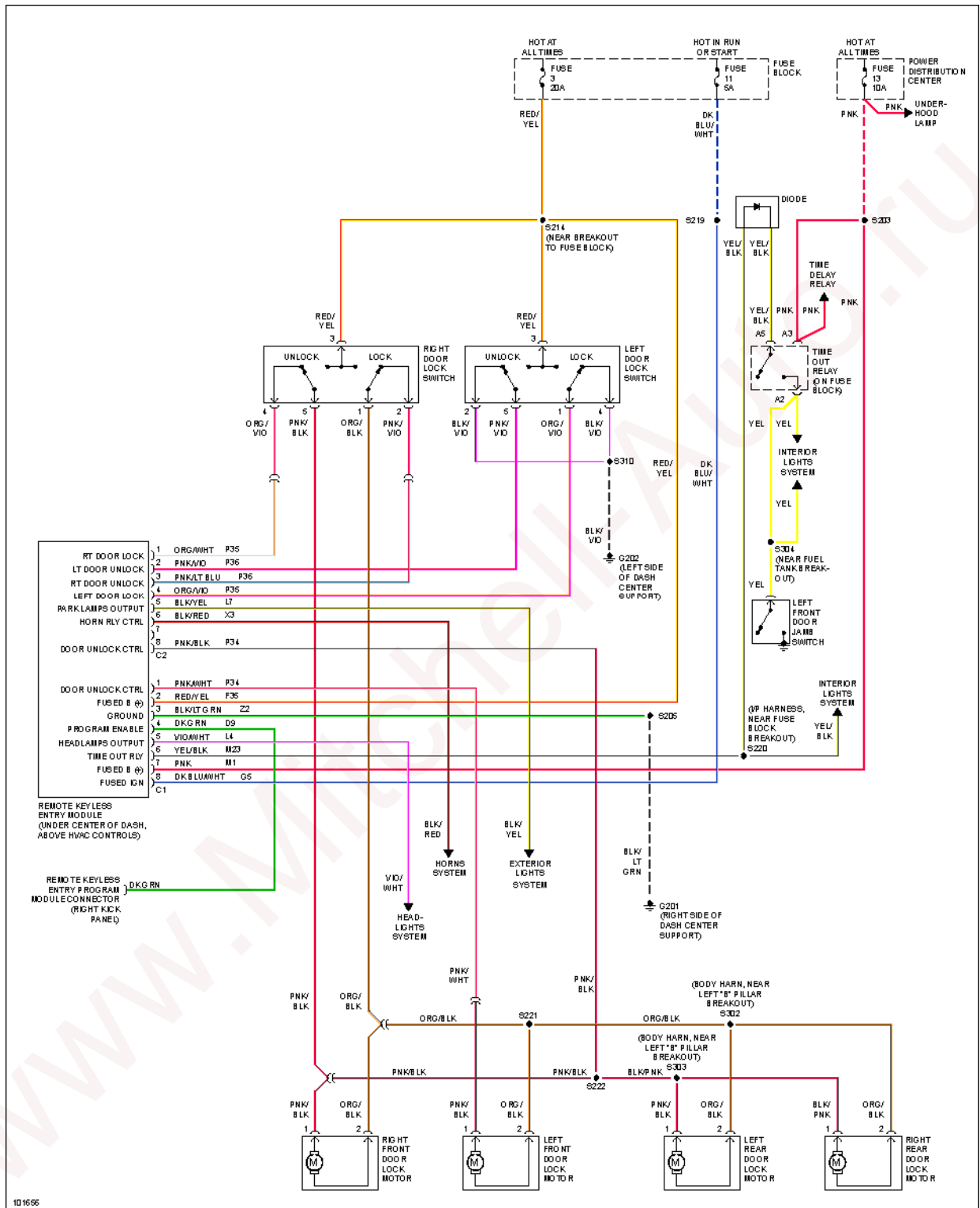


Fig. 25: Keyless Entry Circuit

## POWER MIRRORS

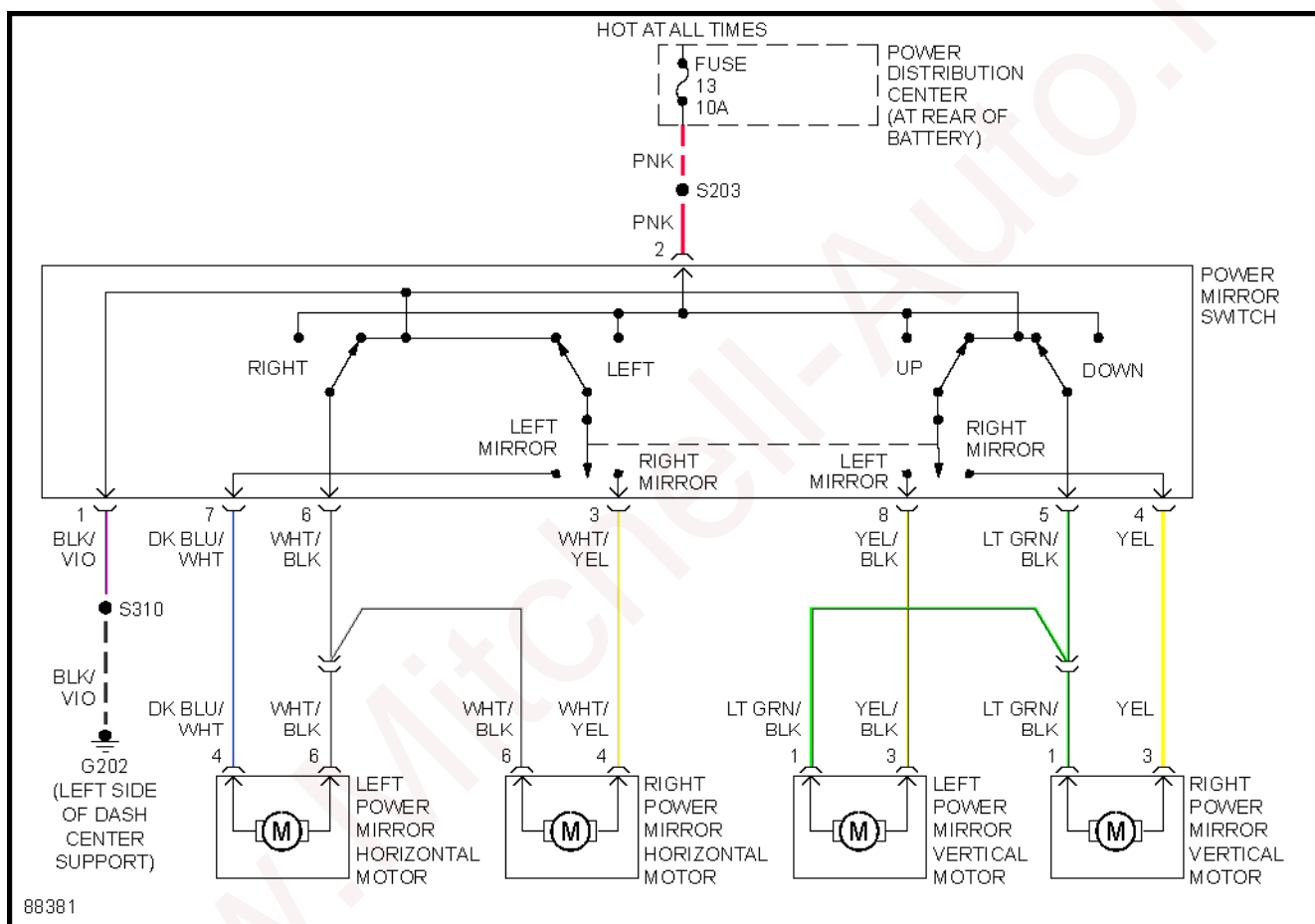


Fig. 26: Power Mirror Circuit

POWER TOP/SUNROOF

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon


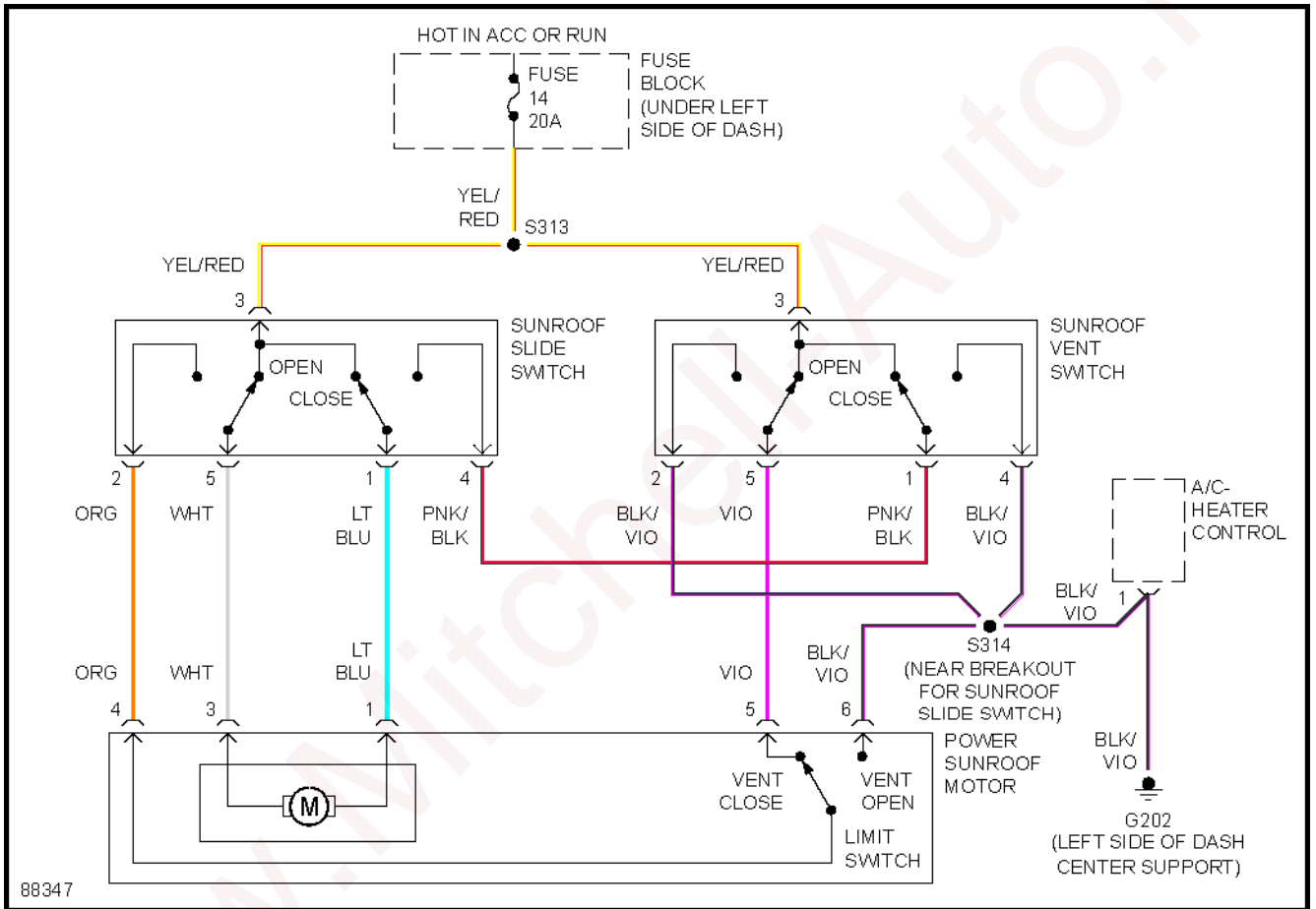


Fig. 27: Power Top/Sunroof Circuits

## POWER WINDOWS

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

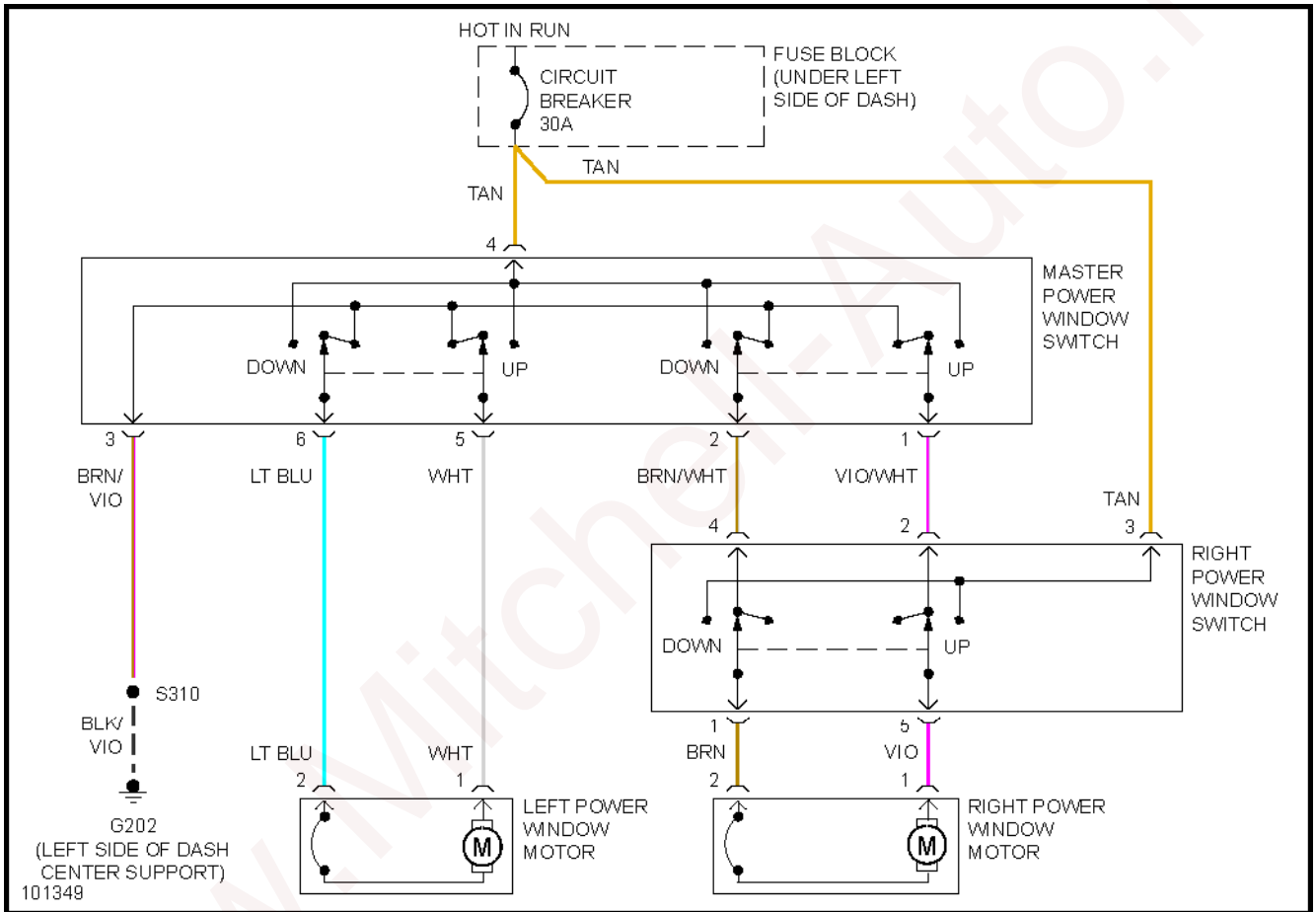

**Fig. 28: Power Window Circuit**

### RADIO

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon


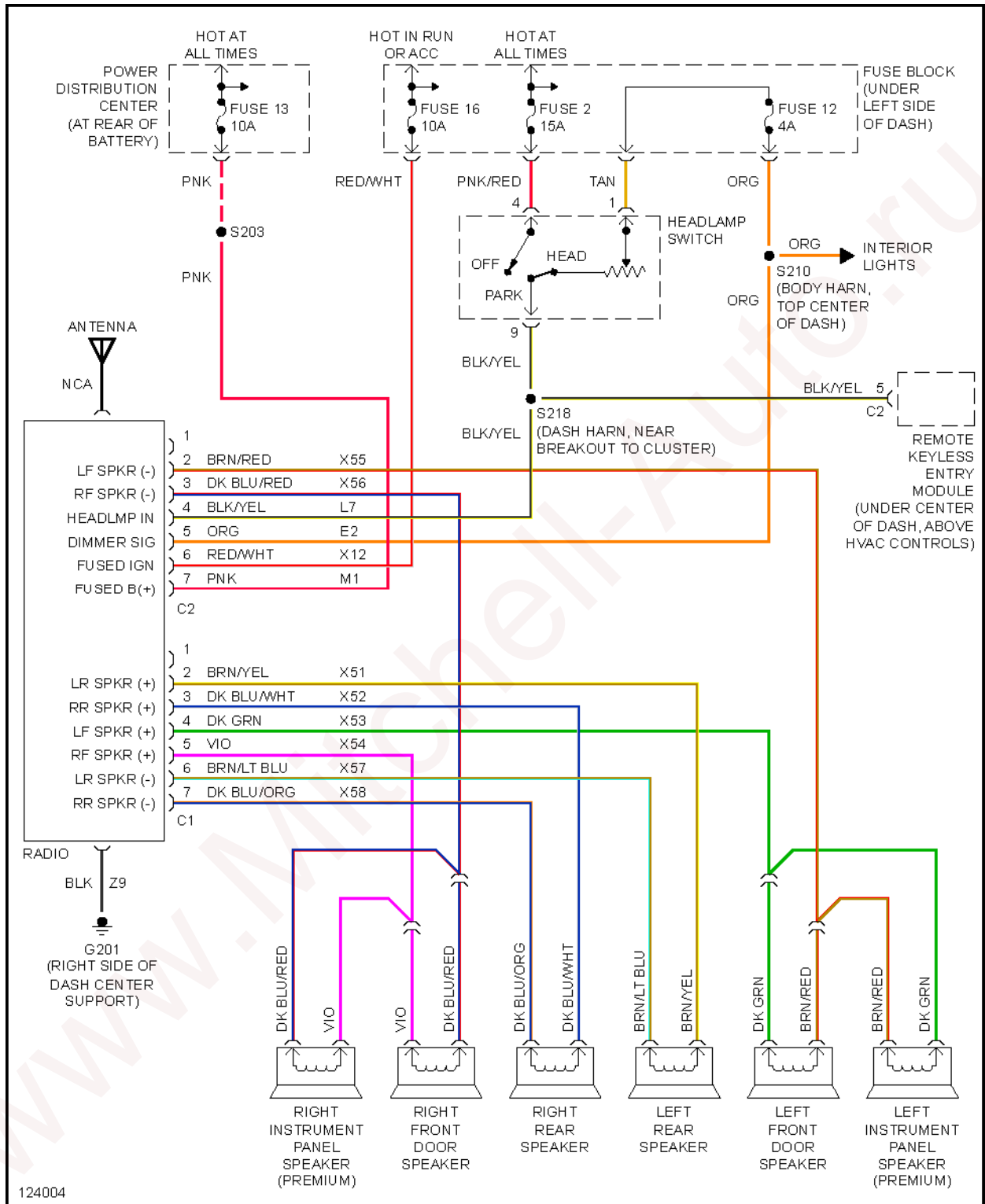


Fig. 29: Radio Circuits

## STARTING/CHARGING

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

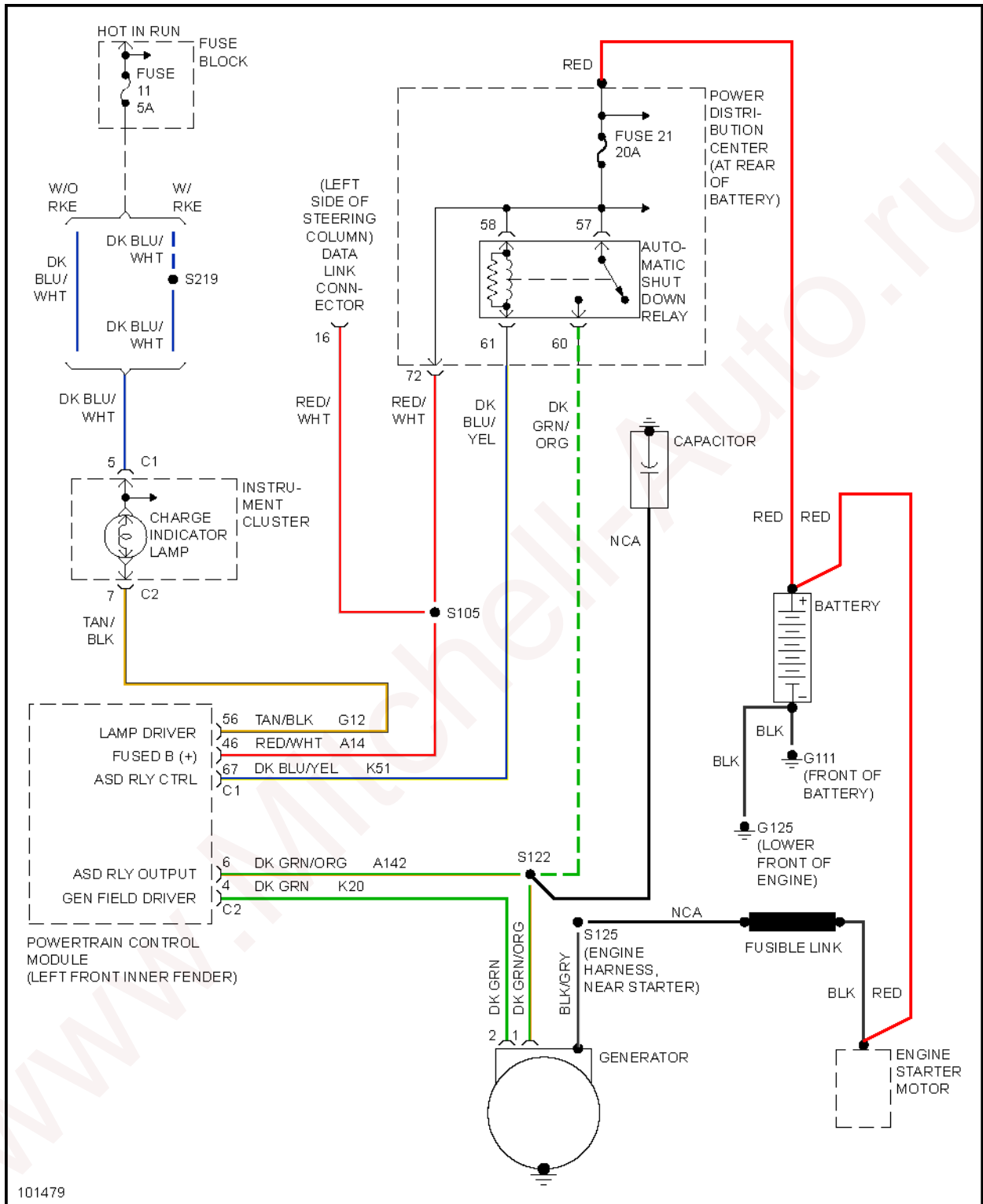

**Fig. 30: Charging Circuit**

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon


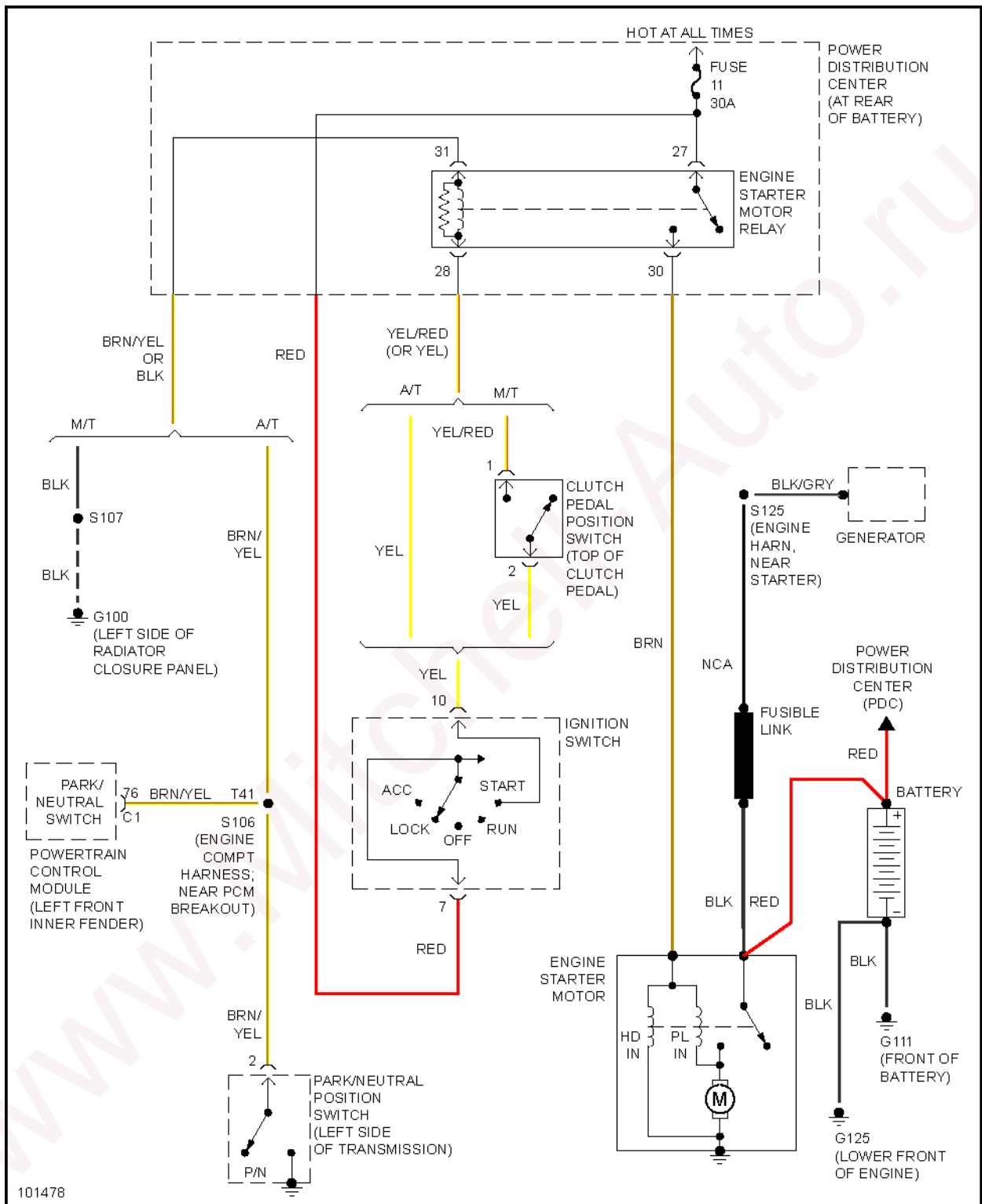


Fig. 31: Starting Circuit

### SUPPLEMENTAL RESTRAINTS

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

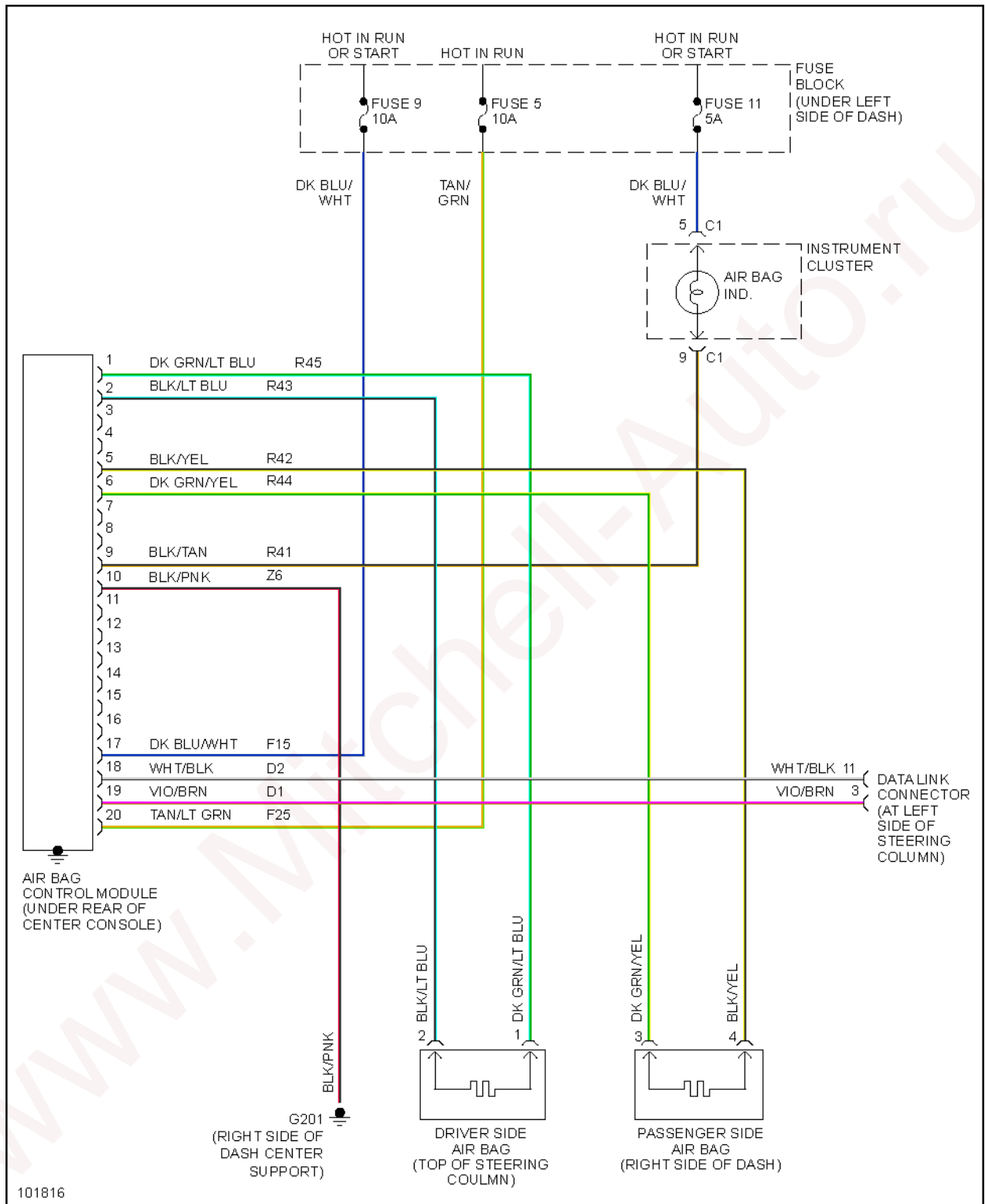


**Fig. 32: Supplemental Restraint Circuit**

## TRANSMISSION



# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

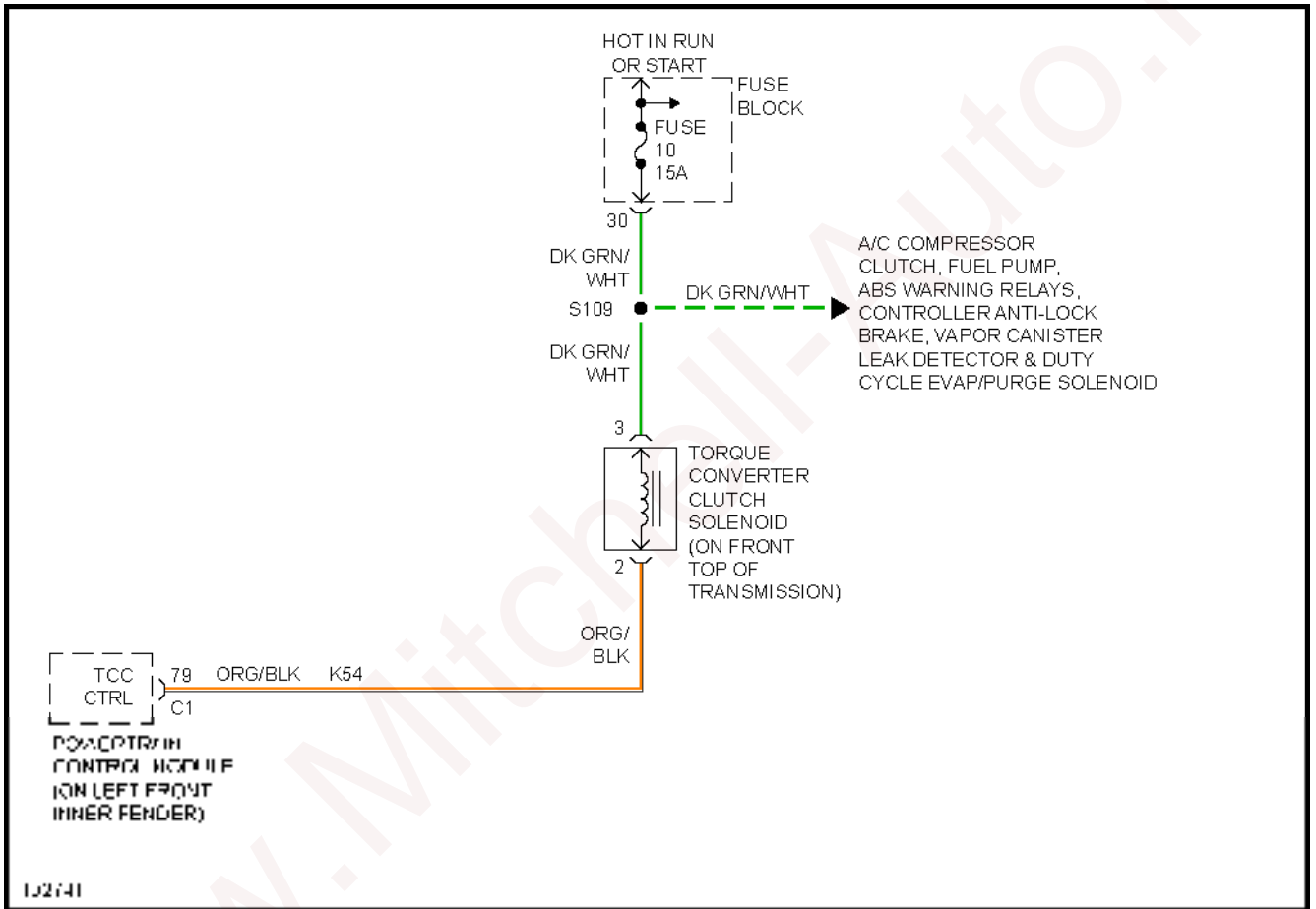

**Fig. 33: Transmission Circuit**

## WARNING SYSTEMS

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon


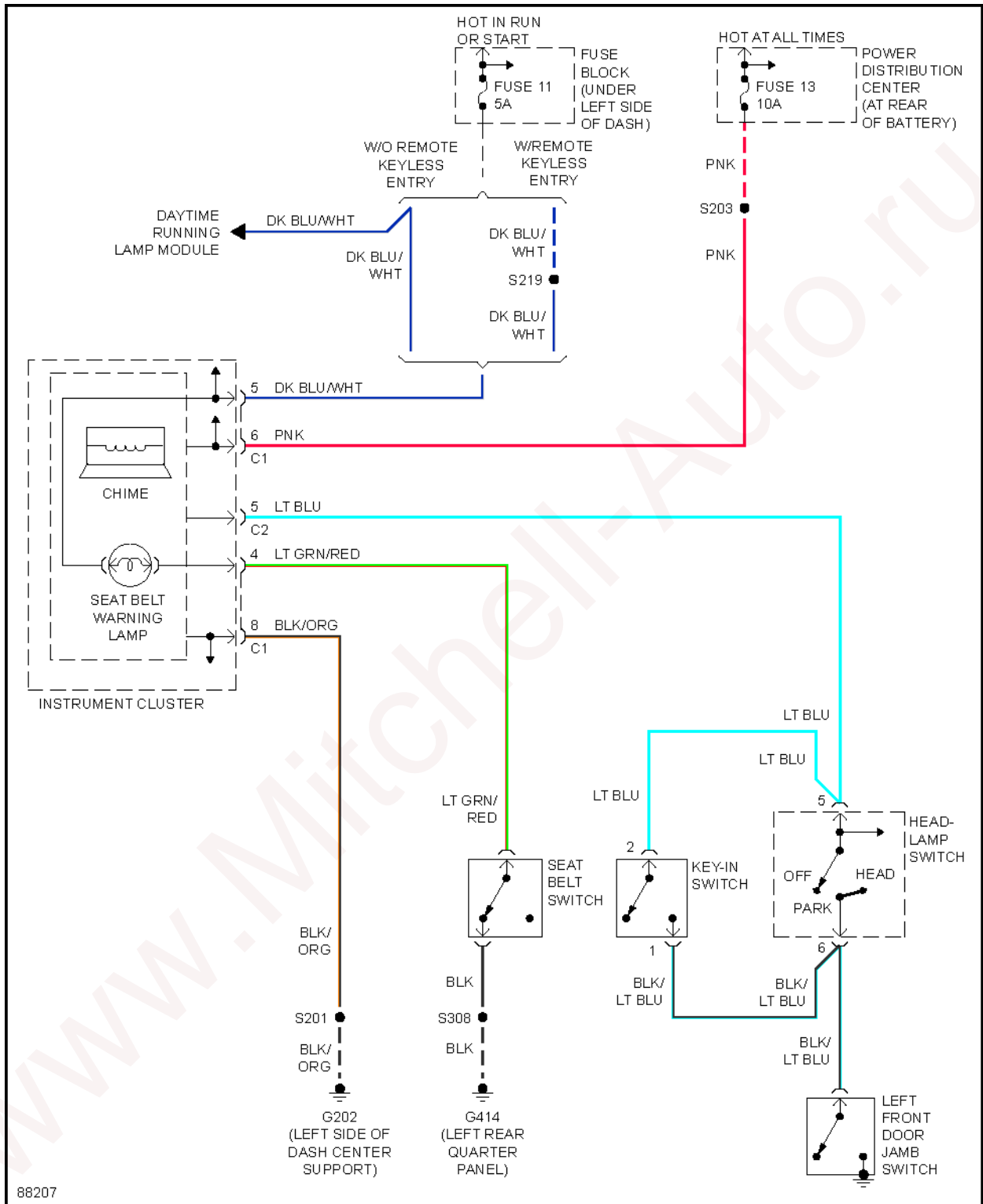


Fig. 34: Warning System Circuits

### WIPER/WASHER

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

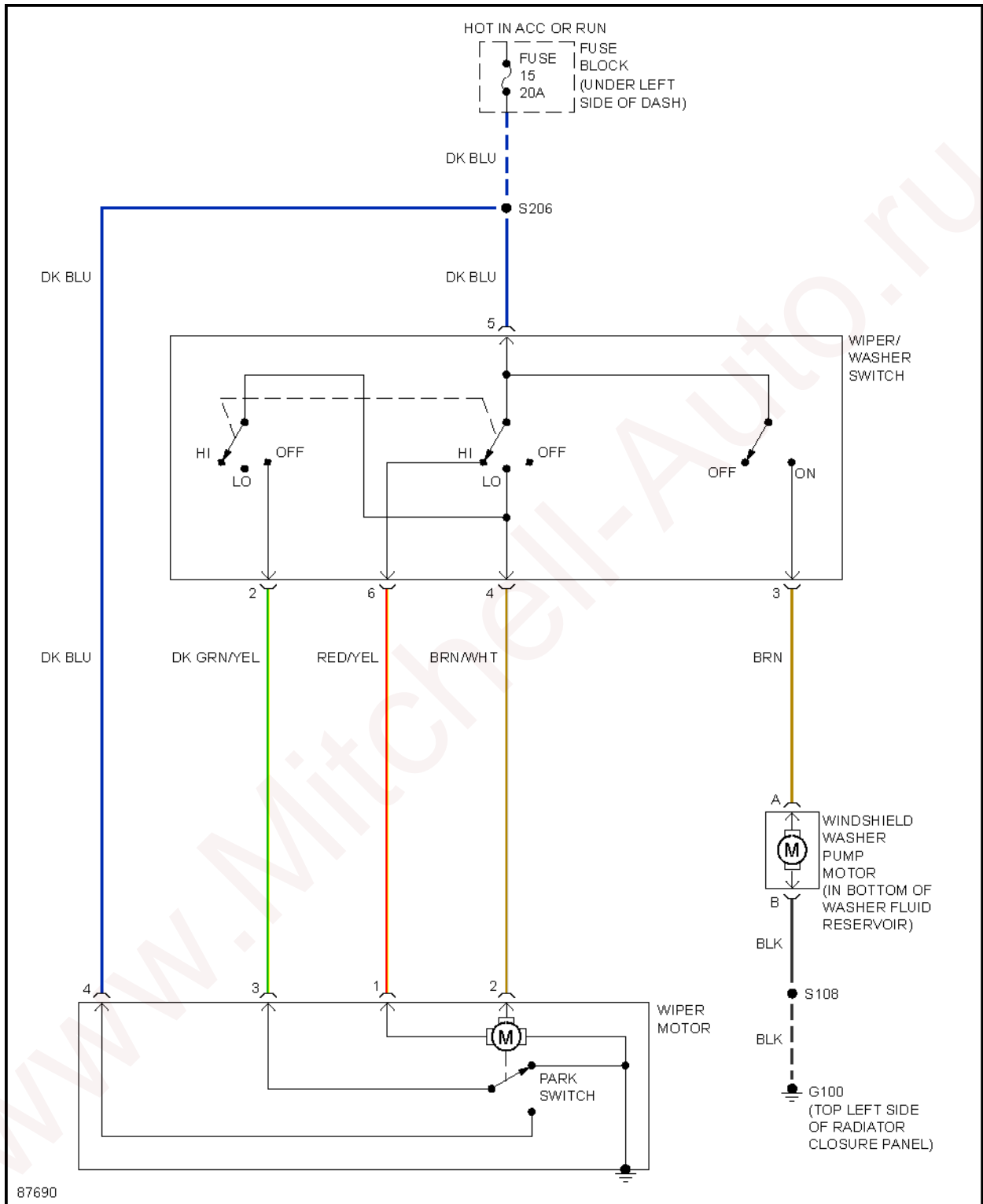

**Fig. 35: 2-Speed Wiper/Washer Circuit**

# 1998 Dodge Neon Sport

## 1998 System Wiring Diagrams Dodge - Neon

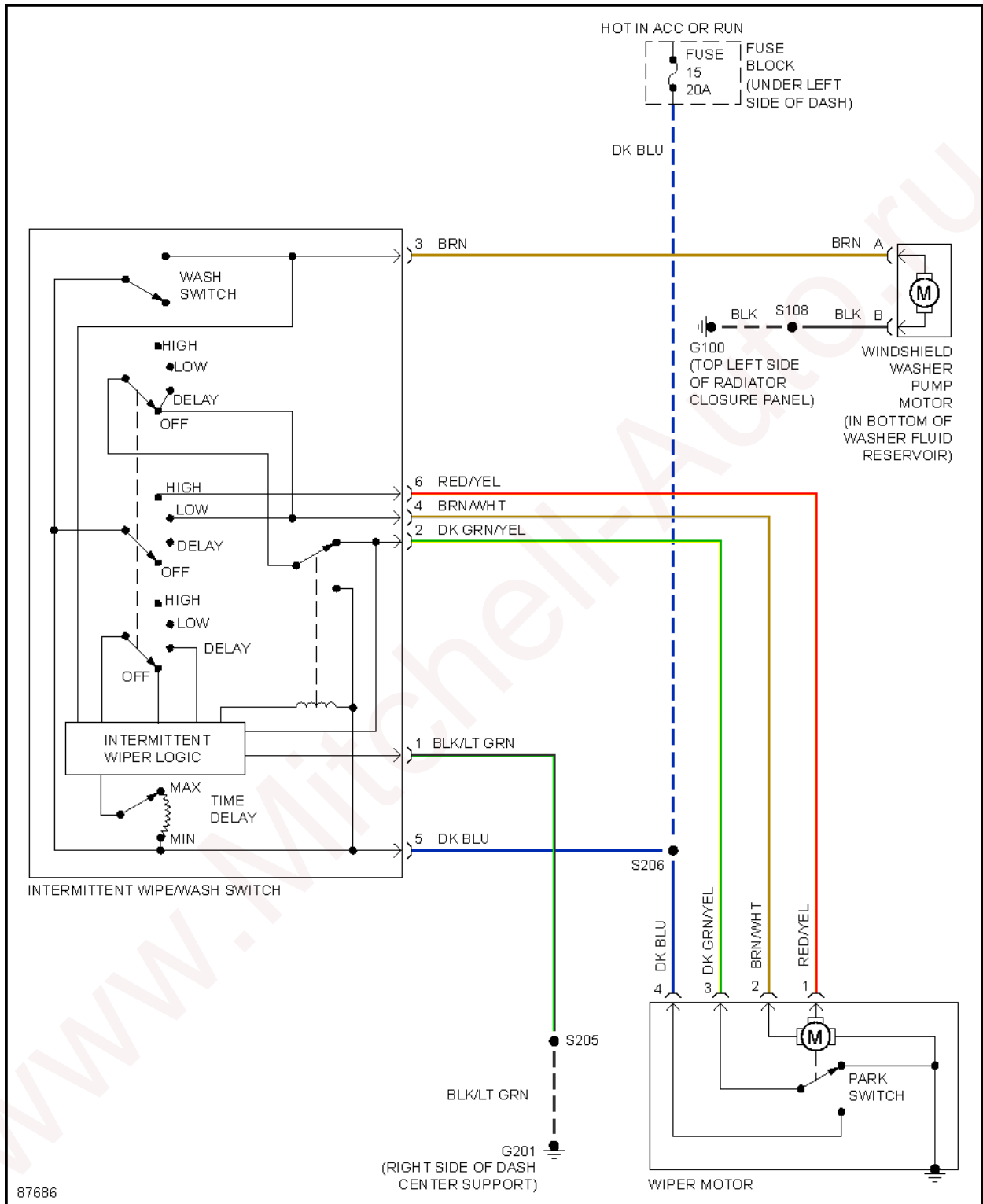


Fig. 36: Interval Wiper/Washer Circuit